

Systems and Devices 1


Lec 3a :

Combinatorial Logic

Before we get started ...


- We live in the fourth generation of computers:
 - ▶ Thermionic valve, Transistor, IC, Micro-processor
- Default technology: transistor, therefore preferred number base: binary, processed using Boolean logic gate.
- How do we process data within our computer?
 - ▶ Identify the state of the computer e.g. what operation it is currently performing, what data has been selected to be processed and what results are produced?

SimpleCPU_v1a

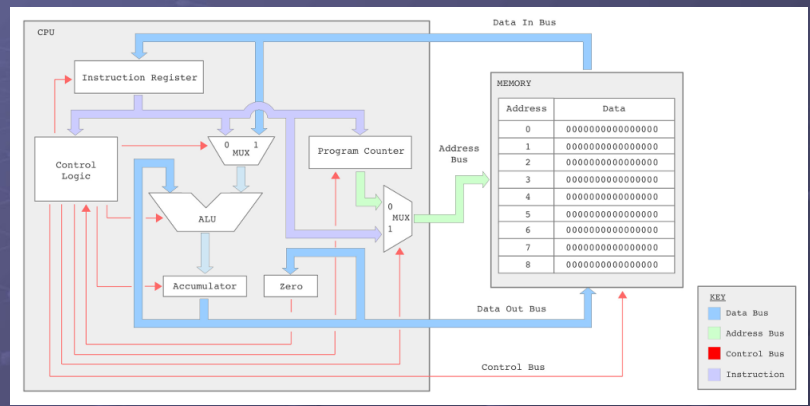


- Block diagram
 - ▶ We need to implement each functional block using logic gates i.e. as combinatorial logic circuits.

SimpleCPU_v1a

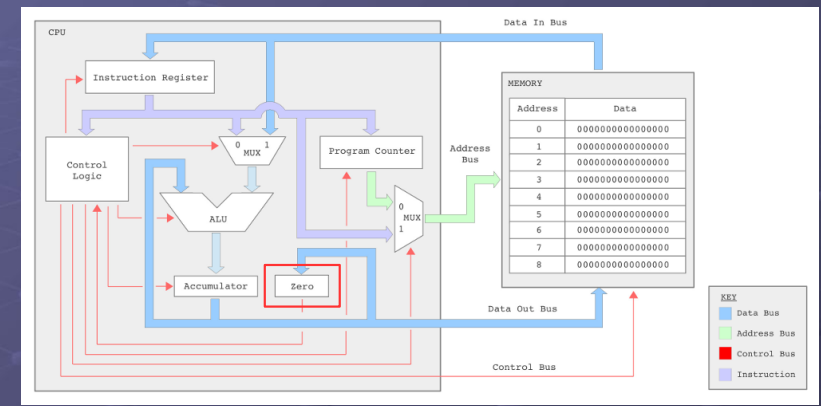

- Block diagram
 - ▶ Status bits : to control the flow of information in a computer we need to test its state i.e. data values.


Logic gates

 

• Quick quizzz: what logic gate could be used to test if :


- ▶ Two bits are equal $A = B$
- ▶ Two bits are both zero $A = B = 0$
- ▶ At least one bit is zero $A = 0 \text{ OR } B = 0$

Example : NOR_8.zip

 


• To test if an 8 bit value is zero we can use an 8 bit NOR gate.

NOR	A	B	Z
	0	0	1
	0	1	0
	1	0	0
	1	1	0

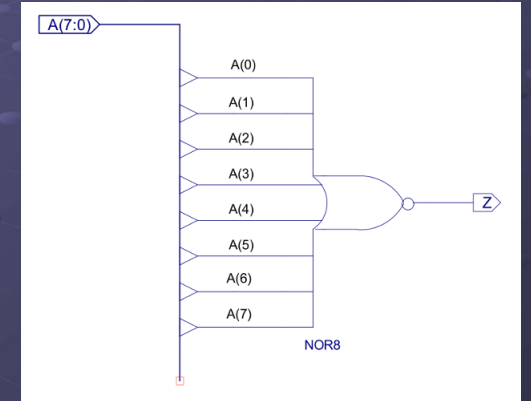


SimpleCPU_v1a

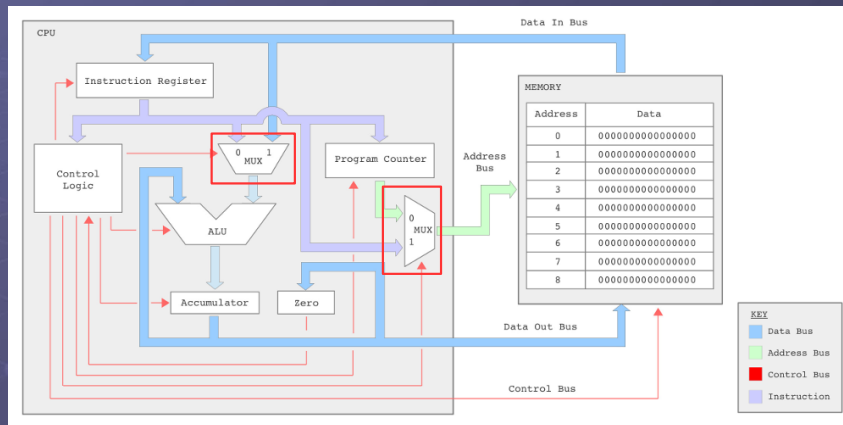


• Block diagram
 ▶ Multiplexer : a core requirement of any computer is to route / move data between functional blocks.

Multiplexers

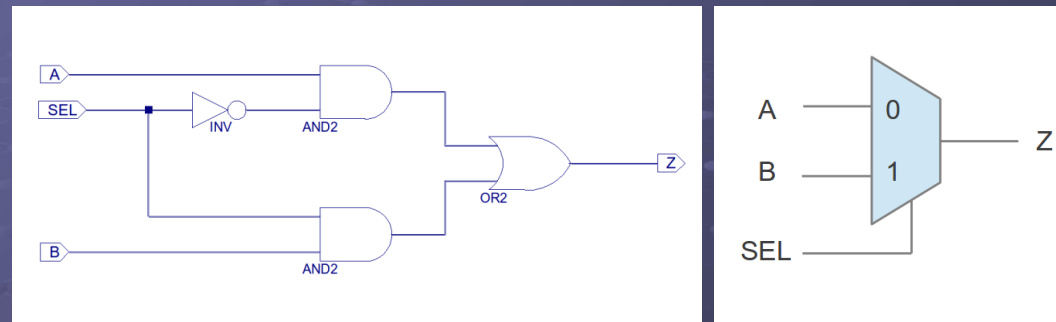

• 2:1 1bit data multiplexer (MUX)
 ▶ Gate level implementation and Circuit Symbol
 ▶ IF SEL = 0 THEN Z = A
 ▶ IF SEL = 1 THEN Z = B


Multiplexers

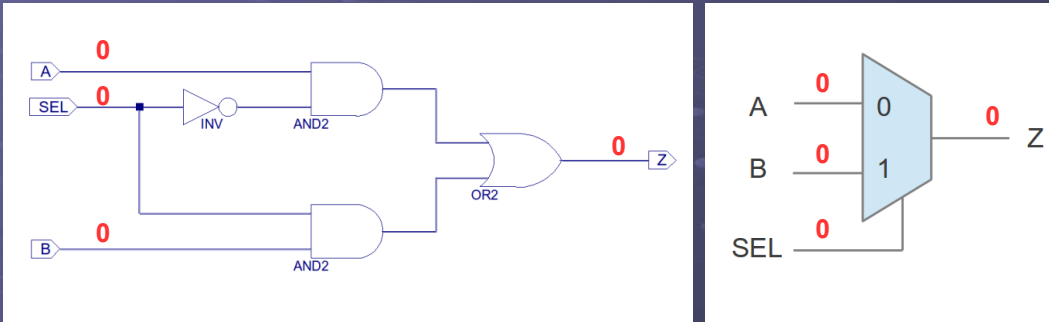

- 2:1 1bit data multiplexer (MUX)
 - ▶ Gate level implementation and Circuit Symbol
 - ▶ IF SEL = 0 THEN Z = A
 - ▶ IF SEL = 1 THEN Z = B

University of York : M Freeman 2021


Multiplexers

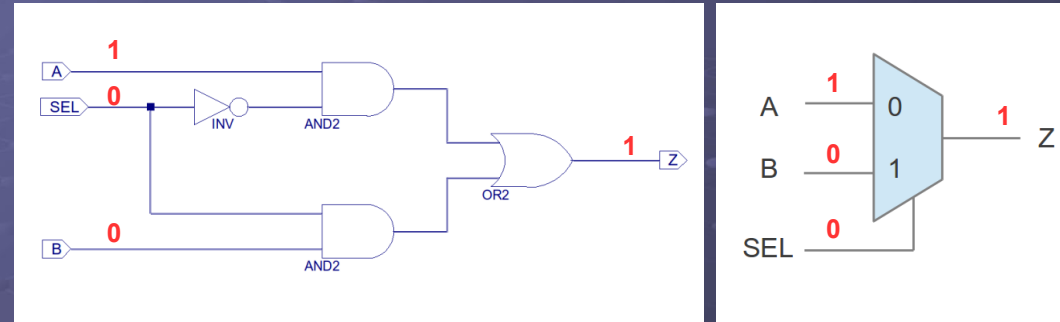

- 2:1 1bit data multiplexer (MUX)
 - ▶ Gate level implementation and Circuit Symbol
 - ▶ IF SEL = 0 THEN Z = A
 - ▶ IF SEL = 1 THEN Z = B

University of York : M Freeman 2021


Multiplexers

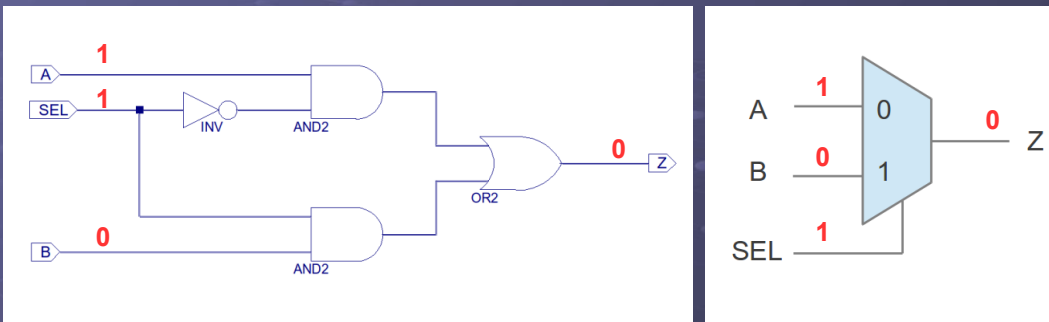

- 2:1 1bit data multiplexer (MUX)
 - ▶ Gate level implementation and Circuit Symbol
 - ▶ IF SEL = 0 THEN Z = A
 - ▶ IF SEL = 1 THEN Z = B

University of York : M Freeman 2021


Multiplexers

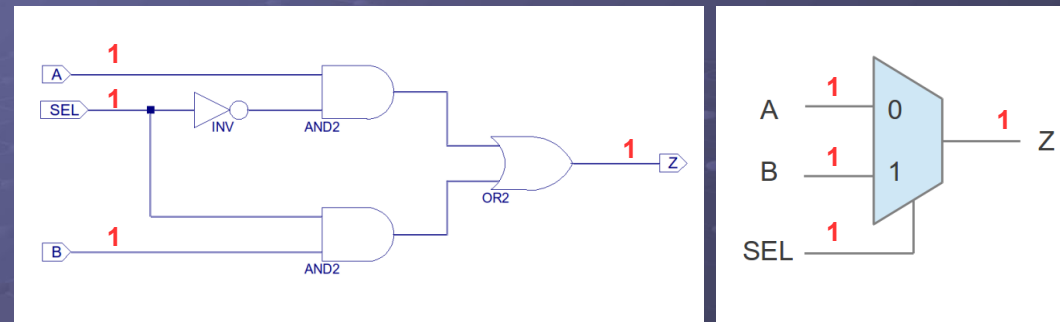

- 2:1 1bit data multiplexer (MUX)
 - ▶ Gate level implementation and Circuit Symbol
 - ▶ IF SEL = 0 THEN Z = A
 - ▶ IF SEL = 1 THEN Z = B

University of York : M Freeman 2021


SimpleCPU_v1a

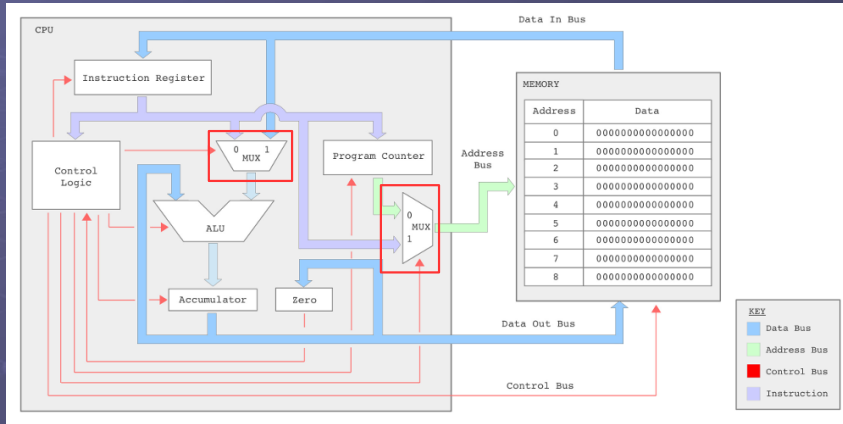

- Problem : the two highlighted multiplexers need to select between two 8 bit values.
 - ▶ May also need to select between more than two input sources.

University of York : M Freeman 2021


Multiplexers

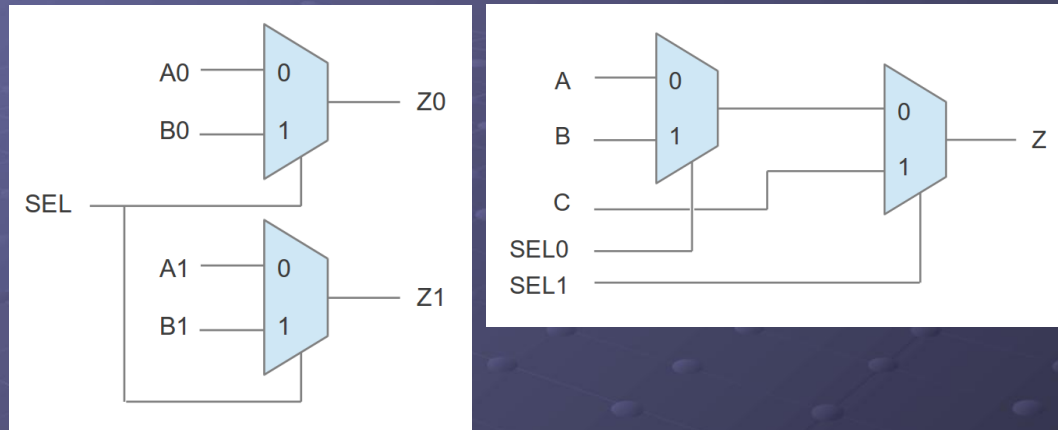

- 2:1 x 2bit MUX: Parallel MUX to increase width
- 3:1 x 1bit MUX: Serial MUX to increase inputs

University of York : M Freeman 2021


Multiplexers

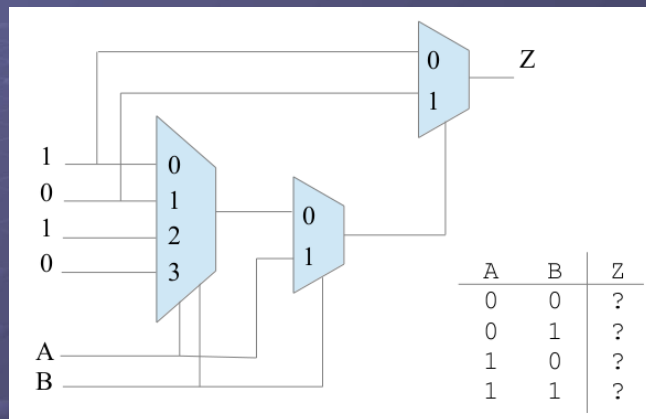

- Quick quiz: complete the truth table
 - ▶ Bonus question : what two logic gates can be used to implement this circuit?


University of York : M Freeman 2021

Example : MUX_2.zip

 


Simulation

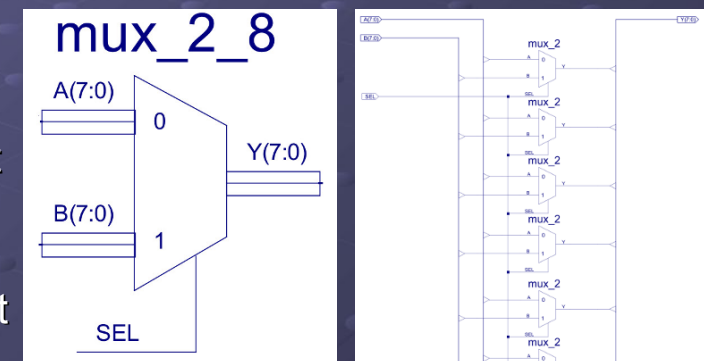- ▶ MUX_2_8 : a two input 8 bit multiplexer
- ▶ MUX_4_8 : a four input 8 bit multiplexer



University of York : M Freeman 2021

SimpleCPU_v1a

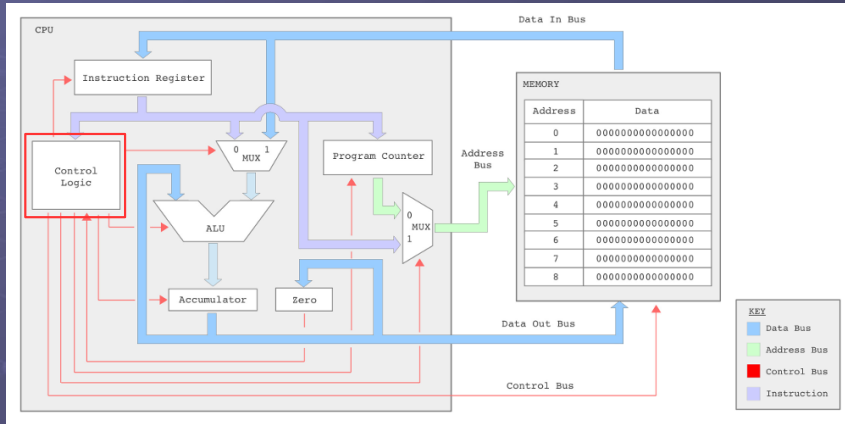

- Block diagram
 - Encoders / Decoders : within the processor information is stored using a range of binary representations.

University of York : M Freeman 2021


Binary encoding

Decimal	Binary	BCD	One-hot
0	0000 0000	0000 0000	0000 0000 0000 0001
1	0000 0001	0000 0001	0000 0000 0000 0010
2	0000 0010	0000 0010	0000 0000 0000 0100
3	0000 0011	0000 0011	0000 0000 0000 1000
4	0000 0100	0000 0100	0000 0000 0001 0000
5	0000 0101	0000 0101	0000 0000 0010 0000
6	0000 0110	0000 0110	0000 0000 0100 0000
7	0000 0111	0000 0111	0000 0000 1000 0000
8	0000 1000	0000 1000	0000 0001 0000 0000
9	0000 1001	0000 1001	0000 0010 0000 0000
10	0000 1010	0001 0000	0000 0100 0000 0000
11	0000 1011	0001 0001	0000 1000 0000 0000
12	0000 1100	0001 0010	0001 0000 0000 0000
13	0000 1101	0001 0011	0010 0000 0000 0000
14	0000 1110	0001 0100	0100 0000 0000 0000
15	0000 1111	0001 0101	1000 0000 0000 0000

- Alternative binary representations : Binary Coded Decimal (BCD) and One-hot encoding.

University of York : M Freeman 2021


Encoder / Decoder

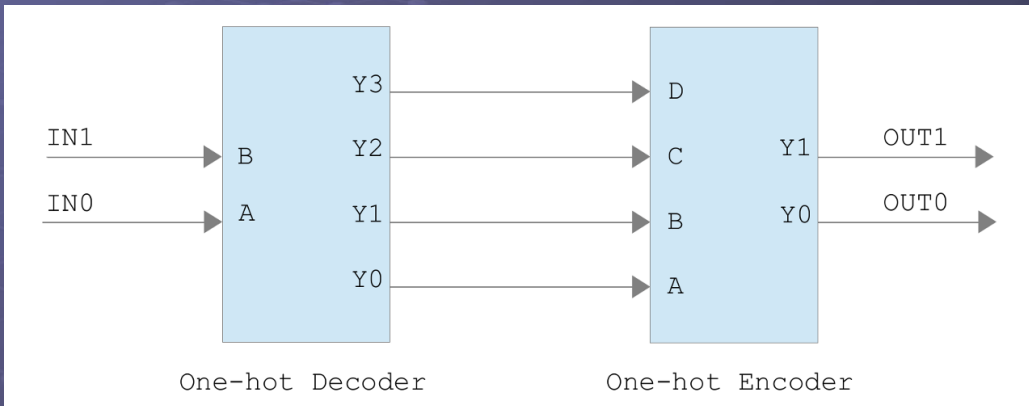

- A two bit binary to One-hot encoder and decoder

University of York : M Freeman 2021


Encoder / Decoder

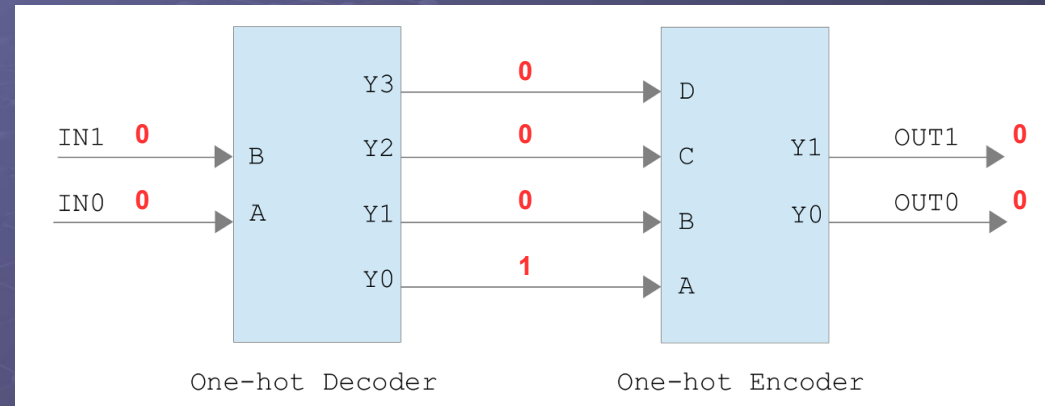

- A two bit binary to One-hot encoder and decoder

University of York : M Freeman 2021


Encoder / Decoder

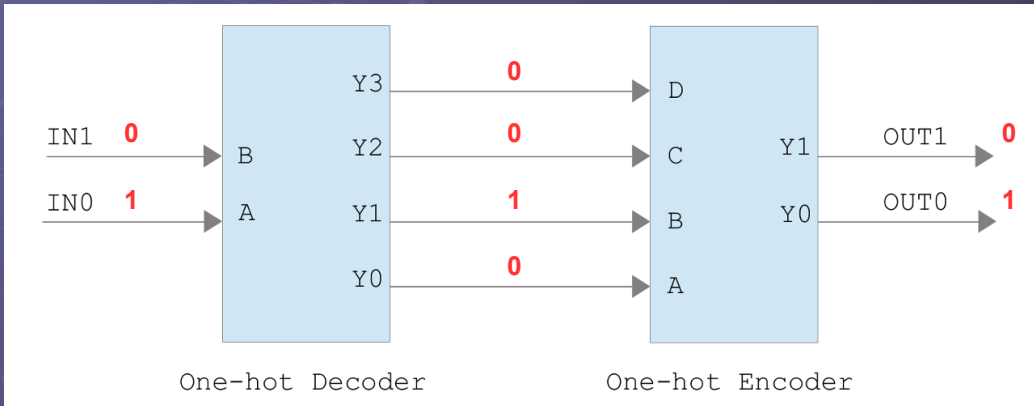

- A two bit binary to One-hot encoder and decoder

University of York : M Freeman 2021


Encoder / Decoder

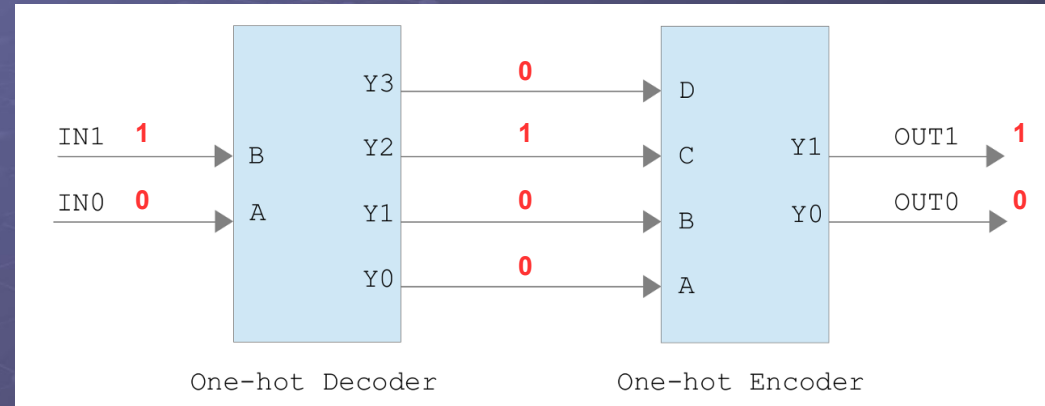

- A two bit binary to One-hot encoder and decoder

University of York : M Freeman 2021



Encoder / Decoder

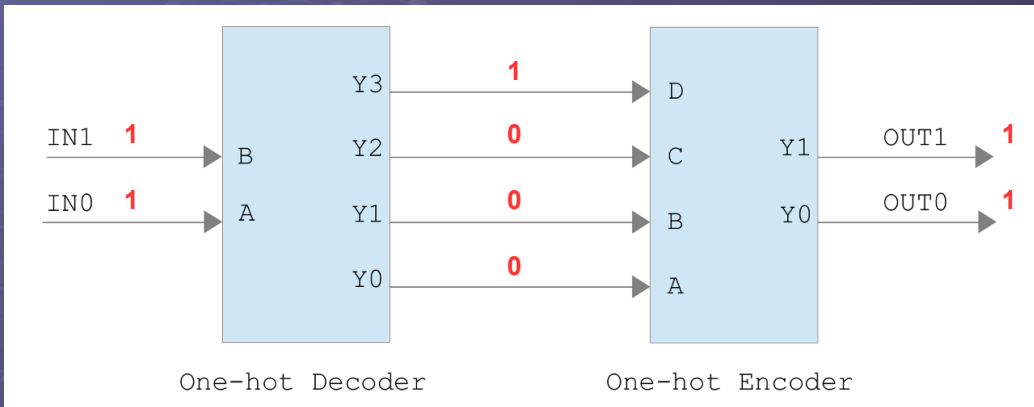

- A two bit binary to One-hot encoder and decoder

University of York : M Freeman 2021

Decoder

 
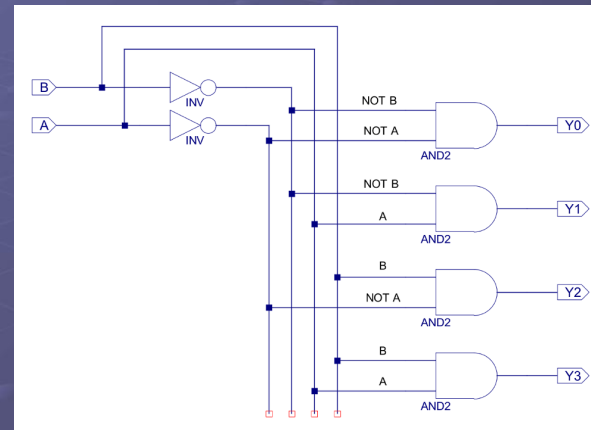


B	A	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- 2bit Binary to One-hot decoder

University of York : M Freeman 2021



Decoder

 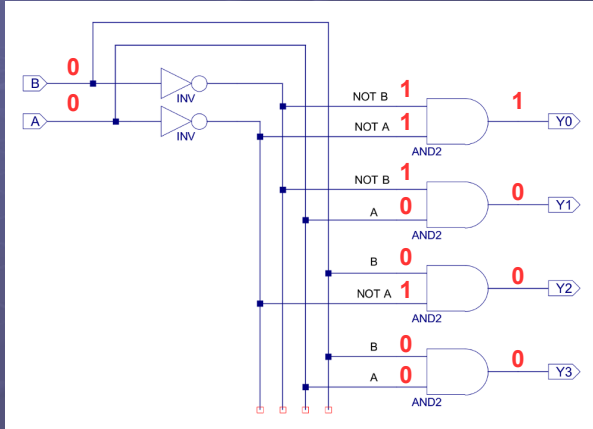

B	A	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

• 2bit Binary to One-hot decoder



Decoder

 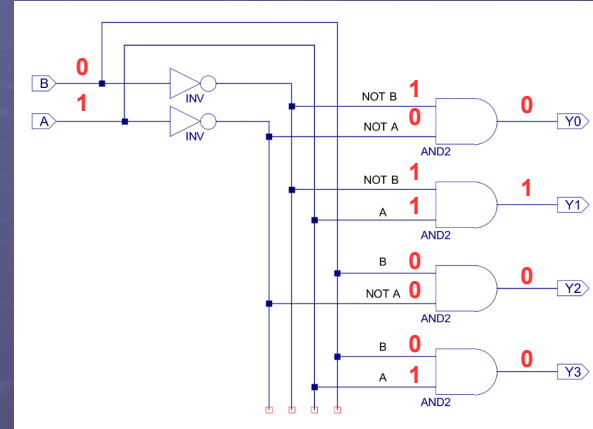

B	A	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

• 2bit Binary to One-hot decoder



Decoder

 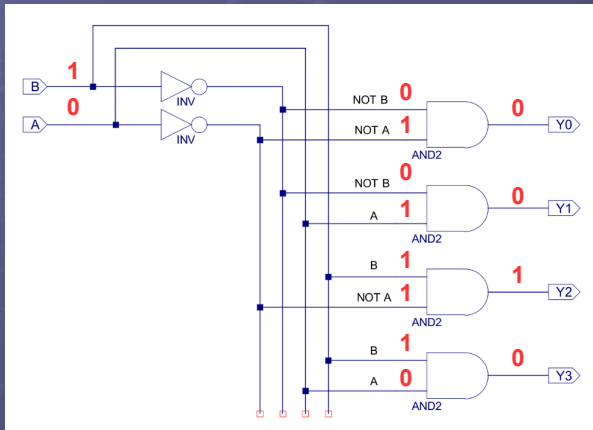

B	A	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

• 2bit Binary to One-hot decoder



Decoder

 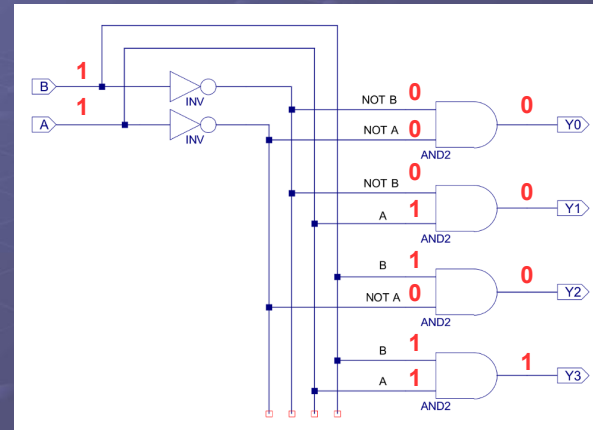

B	A	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

• 2bit Binary to One-hot decoder

Encoder

 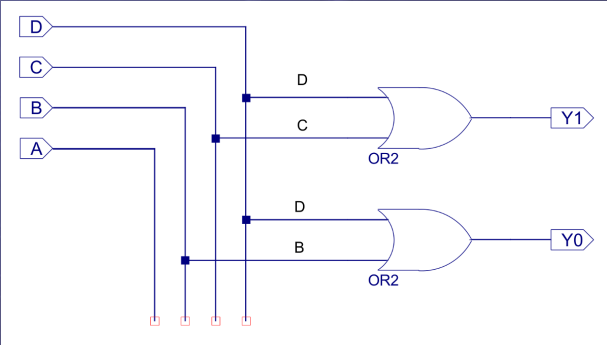



D	C	B	A	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

• 2bit One-hot to Binary encoder

- ▶ One-hot representation simplifies logic design i.e. only 1 bit is ever set.
- ◆ Identify when output is a logic 1 then join active inputs with OR gates.

University of York : M Freeman 2021

Encoder

 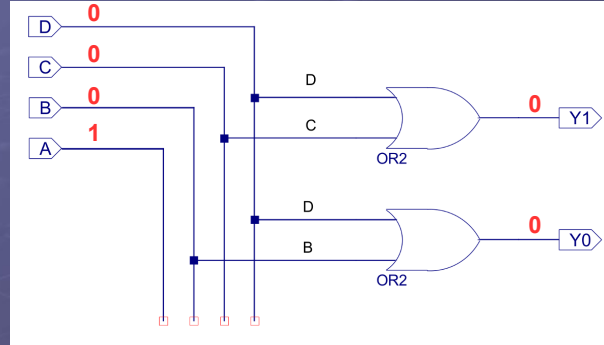



D	C	B	A	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

• 2bit One-hot to Binary encoder

- ▶ One-hot representation simplifies logic design i.e. only 1 bit is ever set.
- ◆ Identify when output is a logic 1 then join active inputs with OR gates.

University of York : M Freeman 2021

Encoder

 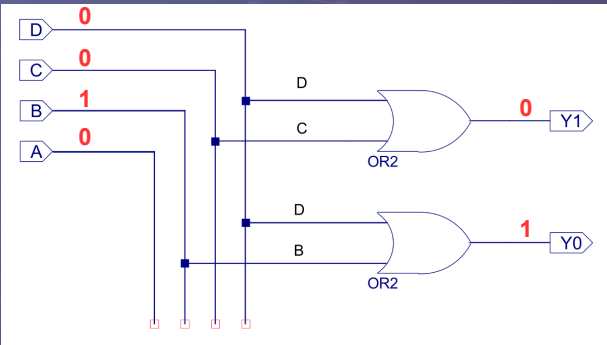



D	C	B	A	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

• 2bit One-hot to Binary encoder

- ▶ One-hot representation simplifies logic design i.e. only 1 bit is ever set.
- ◆ Identify when output is a logic 1 then join active inputs with OR gates.

University of York : M Freeman 2021

Encoder

 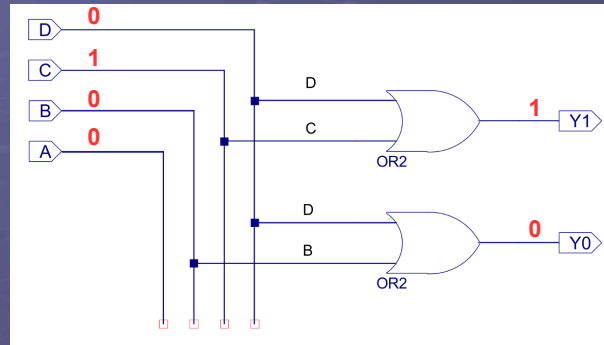



D	C	B	A	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

• 2bit One-hot to Binary encoder

- ▶ One-hot representation simplifies logic design i.e. only 1 bit is ever set.
- ◆ Identify when output is a logic 1 then join active inputs with OR gates.

University of York : M Freeman 2021

Encoder

 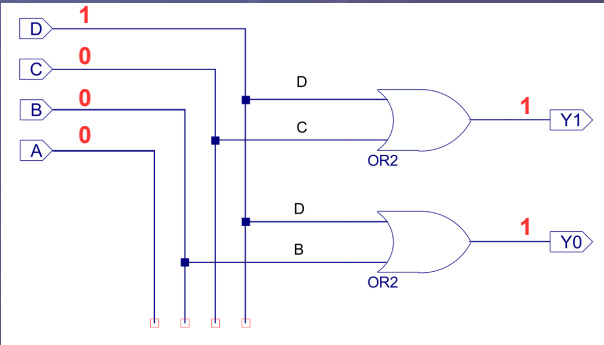

D	C	B	A	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

- 2bit One-hot to Binary encoder
 - ▶ One-hot representation simplifies logic design i.e. only 1 bit is ever set.
 - ◆ Identify when output is a logic 1 then join active inputs with OR gates.

Encoder / Decoder

Which of the following is a valid one-hot value?

- A) 00000000
- B) 01000000
- C) 10000010

An instruction is represented within a computer by a two bit binary number:


- A B
- 0 1 = Add
- 1 0 = Multiply
- A B
- 0 0 = Subtract
- 1 1 = Divide

This two bit code is decoded using the onehot_decoder_4 component to produce control signals S0, S1, S2 and S3. Complete the truth table below, identifying what instruction is being processed.


B	A	S3	S2	S1	S0	Instruction
1	0	0	0	0	1	?
1	1	1	0	0	0	?
0	0	0	0	1	0	?
0	1	0	1	0	0	?
0	1	0	1	0	1	?

- Quick quizzz


Example : onehot_encoder.zip

 

 - Simulation
 - ▶ 2 bit input A, B
 - ▶ 2 bit output Y1, Y0



SimpleCPU_v1a

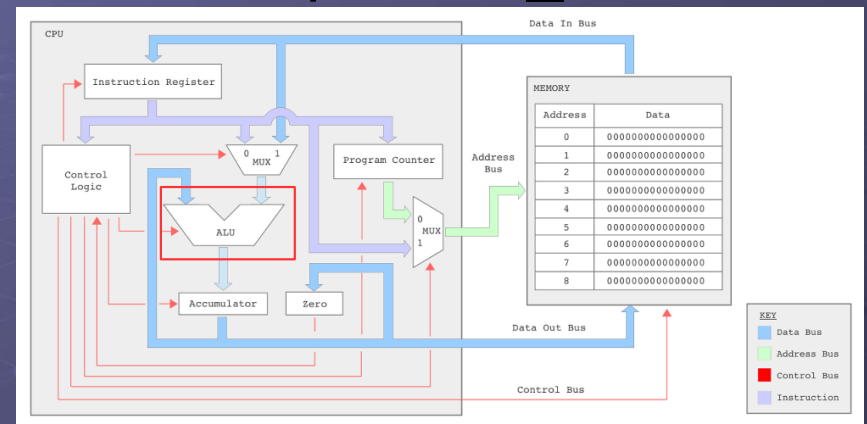

- Block diagram
 - ▶ ALU : a core requirement of any computer is to process data i.e. the Arithmetic and Logic unit, at its heart is the ADDER.

Key skills : working in base 2

$$\begin{array}{r}
 0110101 \\
 +0011100 \\
 \hline
 1 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 53 \\
 +28 \\
 \hline
 1 \\
 \hline
 \end{array}$$

- Adding two binary numbers : $53 + 28$
 - ▶ Positive, integer

University of York : M Freeman 2021

Key skills : working in base 2

$$\begin{array}{r}
 0110101 \\
 +0011100 \\
 \hline
 01 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 53 \\
 +28 \\
 \hline
 01 \\
 \hline
 \end{array}$$

- Adding two binary numbers : $53 + 28$
 - ▶ Positive, integer

University of York : M Freeman 2021

Key skills : working in base 2

$$\begin{array}{r}
 0110101 \\
 +0011100 \\
 \hline
 001 \\
 \hline
 1 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 53 \\
 +28 \\
 \hline
 001 \\
 \hline
 1 \\
 \hline
 \end{array}$$

- Adding two binary numbers : $53 + 28$
 - ▶ Positive, integer

University of York : M Freeman 2021

Key skills : working in base 2

$$\begin{array}{r}
 0110101 \\
 +0011100 \\
 \hline
 0001 \\
 \hline
 11 \\
 \hline
 \end{array}
 \qquad
 \begin{array}{r}
 53 \\
 +28 \\
 \hline
 0001 \\
 \hline
 11 \\
 \hline
 \end{array}$$

- Adding two binary numbers : $53 + 28$
 - ▶ Positive, integer

University of York : M Freeman 2021

Key skills : working in base 2

$$\begin{array}{r}
 0110101 \\
 +0011100 \\
 \hline
 10001 \\
 \hline
 111
 \end{array}
 \qquad
 \begin{array}{r}
 53 \\
 +28 \\
 \hline
 \hline
 \end{array}$$

- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer

University of York : M Freeman 2021

Key skills : working in base 2

$$\begin{array}{r}
 0110101 \\
 +0011100 \\
 \hline
 010001 \\
 \hline
 1111
 \end{array}
 \qquad
 \begin{array}{r}
 53 \\
 +28 \\
 \hline
 \hline
 \end{array}$$

- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer

University of York : M Freeman 2021

Key skills : working in base 2

$$\begin{array}{r}
 0110101 \\
 +0011100 \\
 \hline
 1010001 \\
 \hline
 1111
 \end{array}
 \qquad
 \begin{array}{r}
 53 \\
 +28 \\
 \hline
 81
 \end{array}$$

- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer

University of York : M Freeman 2021


Binary addition

$$\begin{array}{r}
 0110101 \quad \text{A} \quad 53 \\
 +0011100 \quad \text{B} \quad +28 \\
 \hline
 1010001 \quad \text{Sum} \quad 1 \\
 \hline
 1111 \quad \text{Cin} \\
 \text{Cout}
 \end{array}$$

- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer


University of York : M Freeman 2021

Binary addition

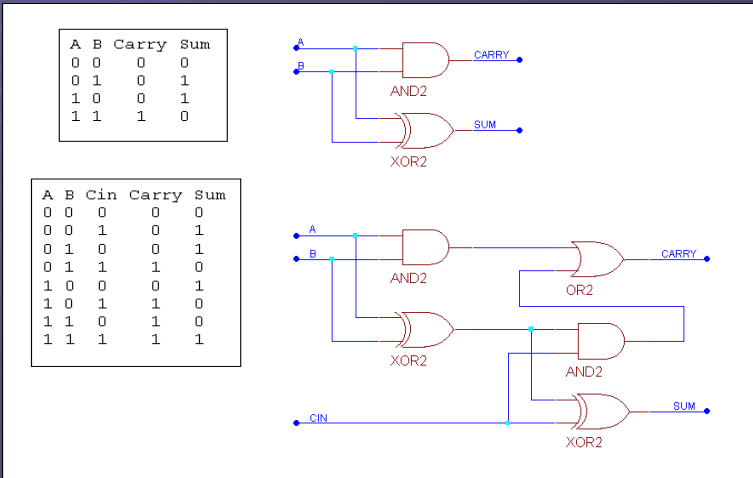


- Half and full adder
 - ▶ Basic components can be combined into larger circuits

Binary addition

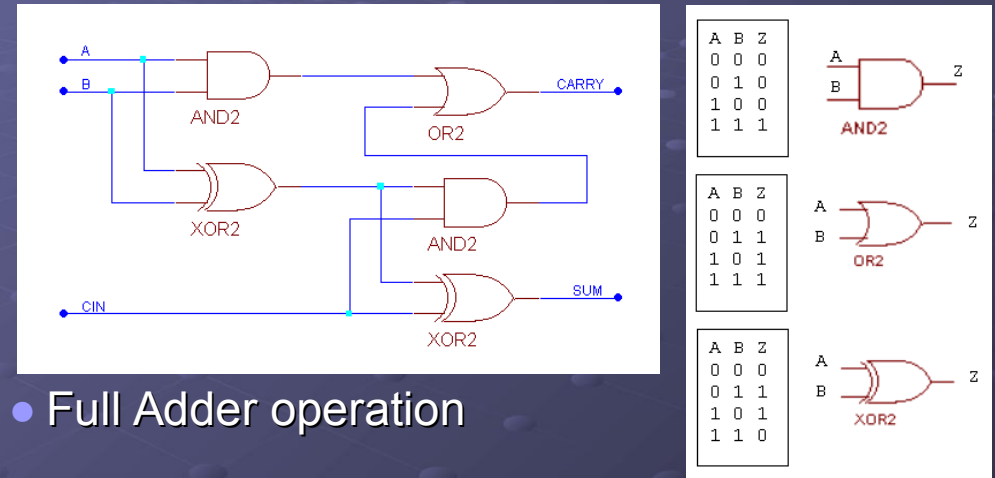


- Full Adder operation

Binary addition

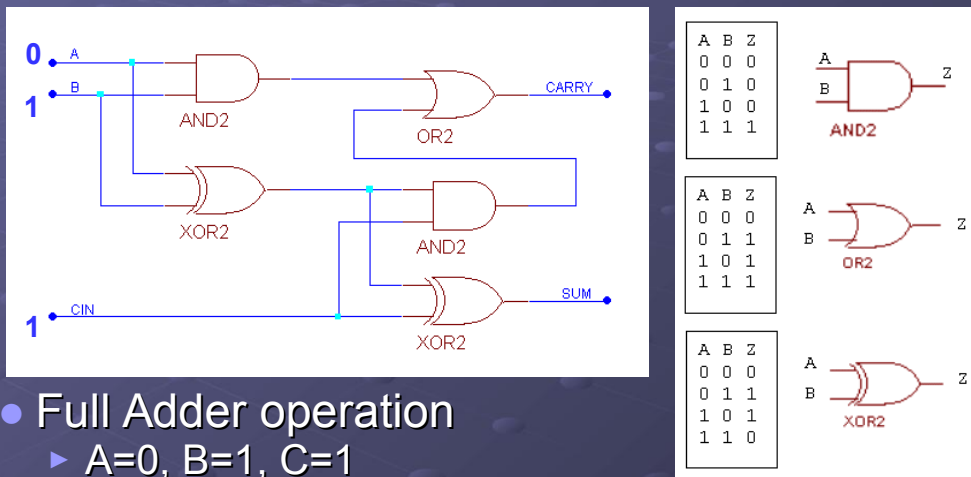


- Full Adder operation
 - ▶ A=0, B=1, C=1

Binary addition

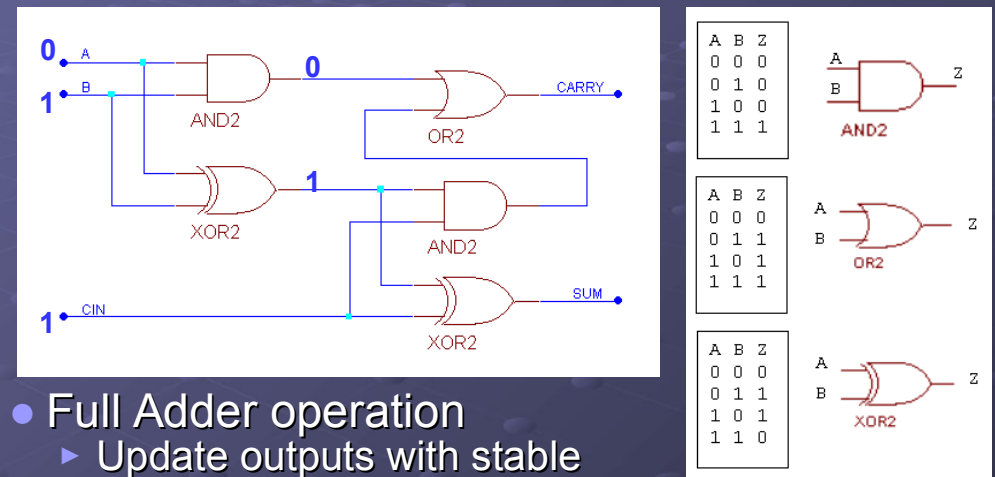

- Full Adder operation
 - ▶ Update outputs with stable values

Binary addition

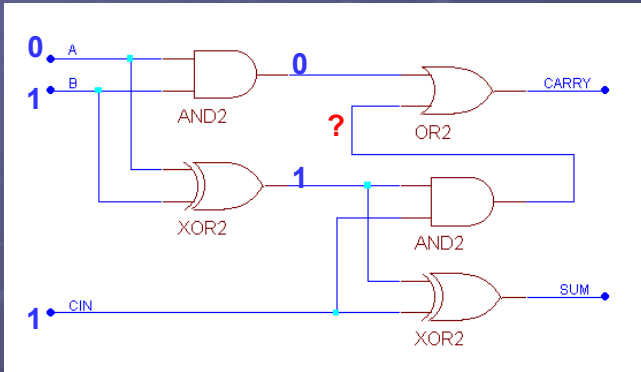

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1


A B Z
0 0 0
0 1 1
1 0 1
1 1 1

A B Z
0 0 0
0 1 1
1 0 1
1 1 1

A B Z
0 0 0
0 1 1
1 0 1
1 1 0

- Full Adder operation
 - ▶ If input not known, trace signal back to source

Binary addition

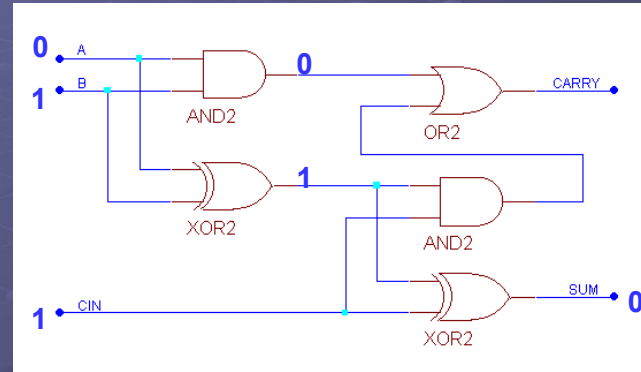

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1


A B Z
0 0 0
0 1 1
1 0 1
1 1 1

A B Z
0 0 0
0 1 1
1 0 1
1 1 1

A B Z
0 0 0
0 1 1
1 0 1
1 1 0

- Full Adder operation
 - ▶ Update outputs with stable values

Binary addition

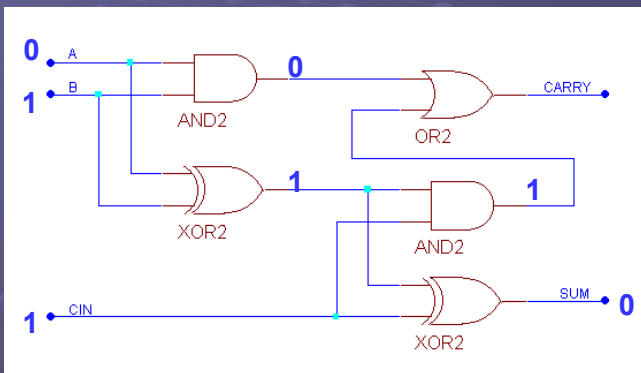

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1


A B Z
0 0 0
0 1 1
1 0 1
1 1 1

A B Z
0 0 0
0 1 1
1 0 1
1 1 1

A B Z
0 0 0
0 1 1
1 0 1
1 1 0

- Full Adder operation
 - ▶ Update outputs with stable values

Binary addition

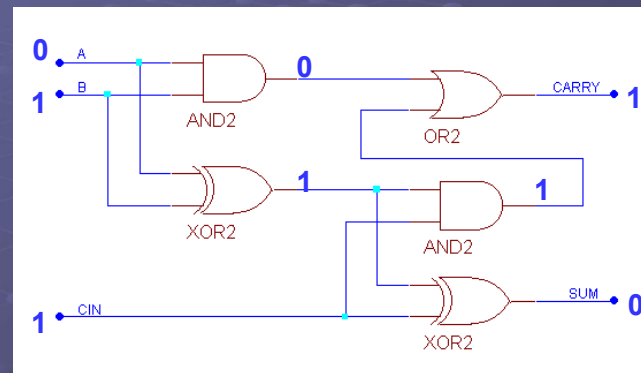

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1


A B Z
0 0 0
0 1 1
1 0 1
1 1 1

A B Z
0 0 0
0 1 1
1 0 1
1 1 1

A B Z
0 0 0
0 1 1
1 0 1
1 1 0

- Full Adder operation
 - ▶ A=0, B=1, C=1
 - ▶ Sum=0, Carry=1

Binary addition

 

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1


A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

- Important limitation : critical path
 - ▶ Worst case delay path, a signal needs to travel through three gate to produce a stable output.

University of York : M Freeman 2021

Binary addition

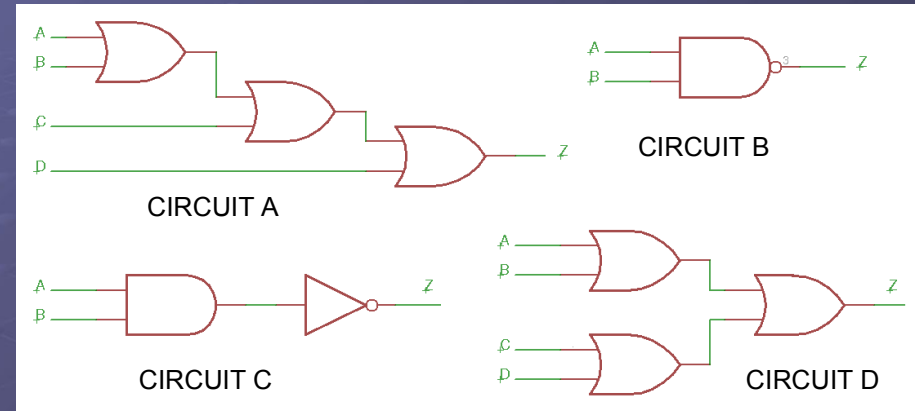

- Quick Quizzz
 - ▶ Which rank these circuits in order of critical path delay, quickest to slowest.

University of York : M Freeman 2021

Summary

- Key concepts :
 - ▶ Fundamental building blocks of a computer:
 - ◆ Multiplexer (bit and byte), Encoder, Decoder, Adder ...
 - ▶ Binary encodings
 - ◆ Binary, BCD, One-hot, Gray code ...
 - Link : https://en.wikipedia.org/wiki/Gray_code
 - ▶ Binary arithmetic
 - ◆ Half adder, Full adder, Ripple adder, Carry, Overflow.
 - ◆ Hardware limitations : Critical Path Delay (CPD)
 - Each logic gate will take some time to update its output for a change on its input i.e. propagation delay.
 - ▶ Operation of simple combinatorial logic circuits

University of York : M Freeman 2021