

Systems and Devices 1


Lec 3a :

Combinatorial Logic

Before we get started ...

- We live in the fourth generation of computers:
 - ▶ Thermionic valve, Transistor, IC, Micro-processor
- Default technology: transistor, therefore preferred number base: binary, processed using Boolean logic gate.
- How do we process data within our computer?
 - ▶ Identify the state of the computer e.g. what operation it is currently performing, what data has been selected to be processed and what results are produced?


SimpleCPU_v1a

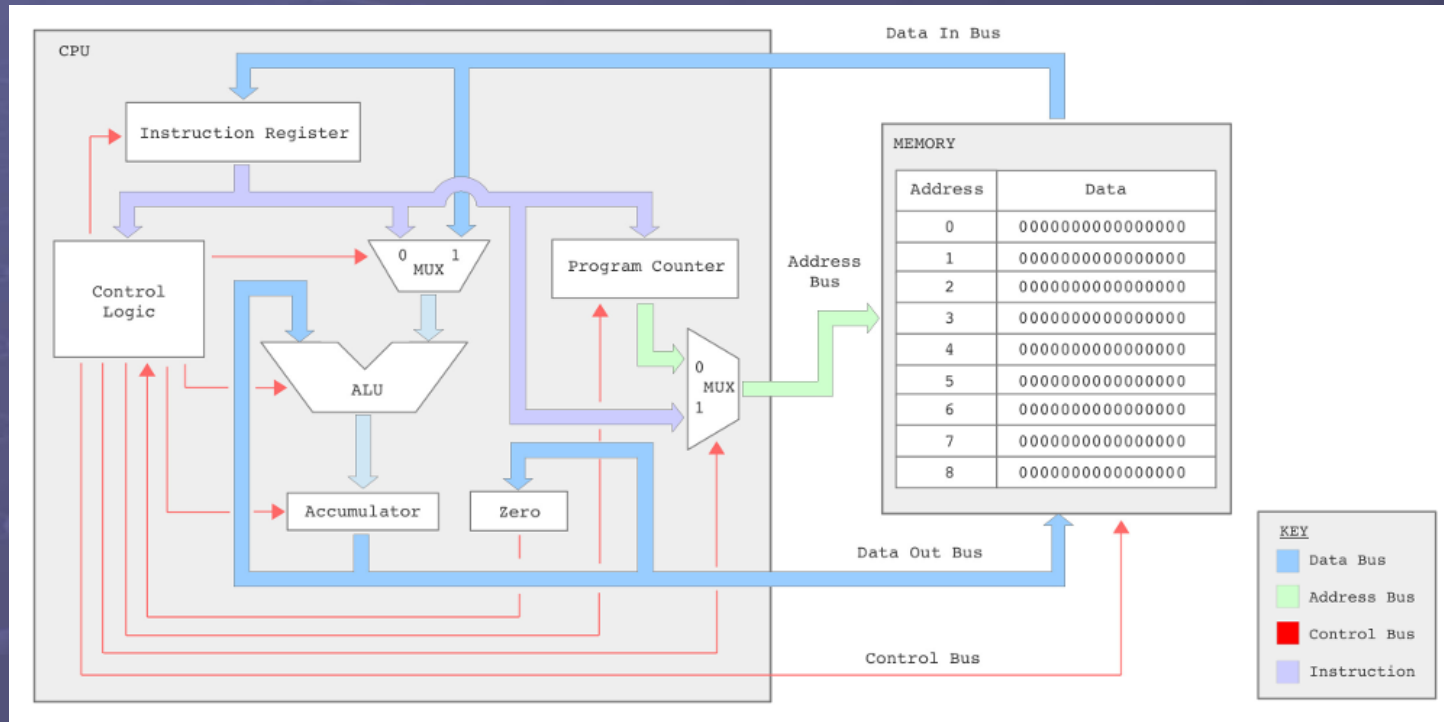

- Block diagram

- ▶ We need to implement each functional block using logic gates i.e. as combinatorial logic circuits.

SimpleCPU_v1a

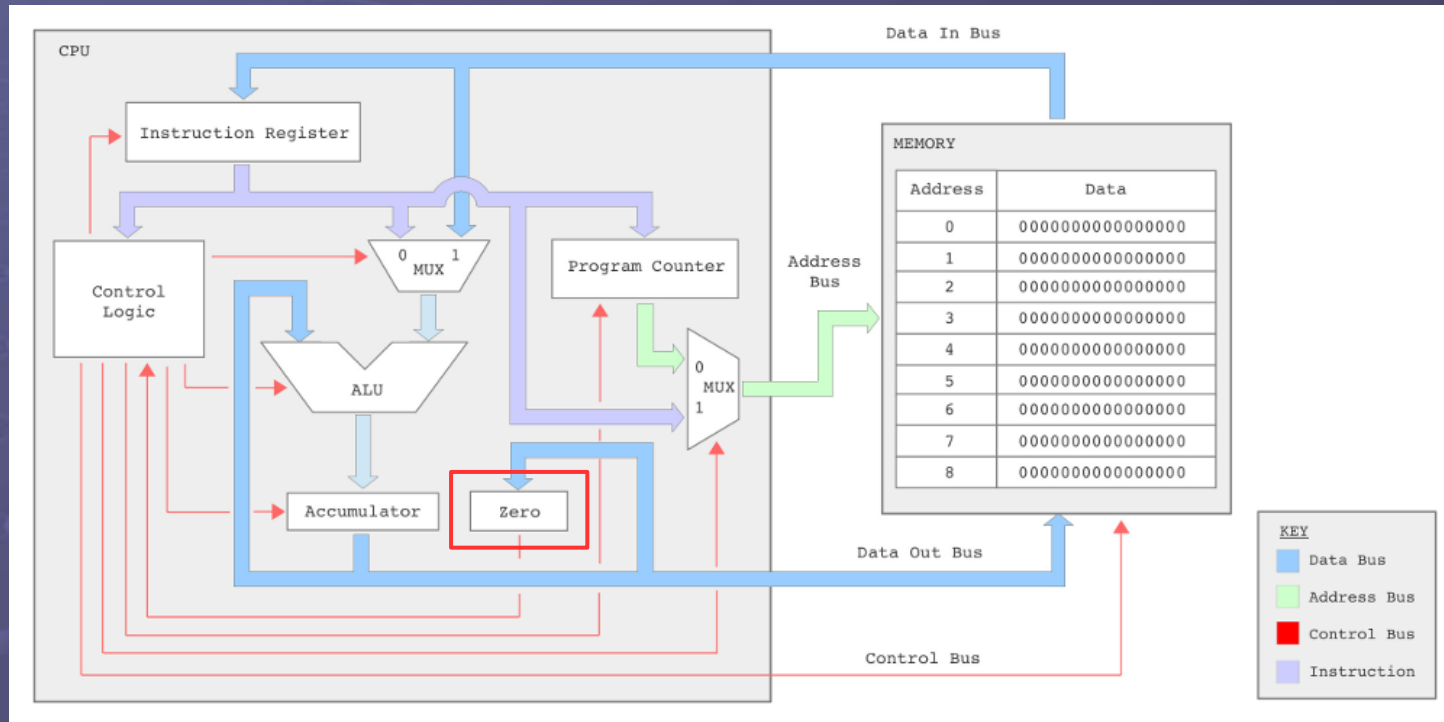


- Block diagram

- ▶ Status bits : to control the flow of information in a computer we need to test its state i.e. data values.

Logic gates



NAND	A	B	Z
	0	0	1
	0	1	1
	1	0	1
	1	1	0

 


NOR	A	B	Z
	0	0	1
	0	1	0
	1	0	0
	1	1	0



XNOR	A	B	Z
	0	0	1
	0	1	0
	1	0	0
	1	1	1


- Quick quizzz: what logic gate could be used to test if :
 - ▶ Two bits are equal $A = B$
 - ▶ Two bits are both zero $A = B = 0$
 - ▶ At least one bit is zero $A = 0 \text{ OR } B = 0$

Example : NOR_8.zip

 


- To test if an 8 bit value is zero we can use an 8 bit NOR gate.

NOR	A	B	Z
	0	0	1
	0	1	0
	1	0	0
	1	1	0

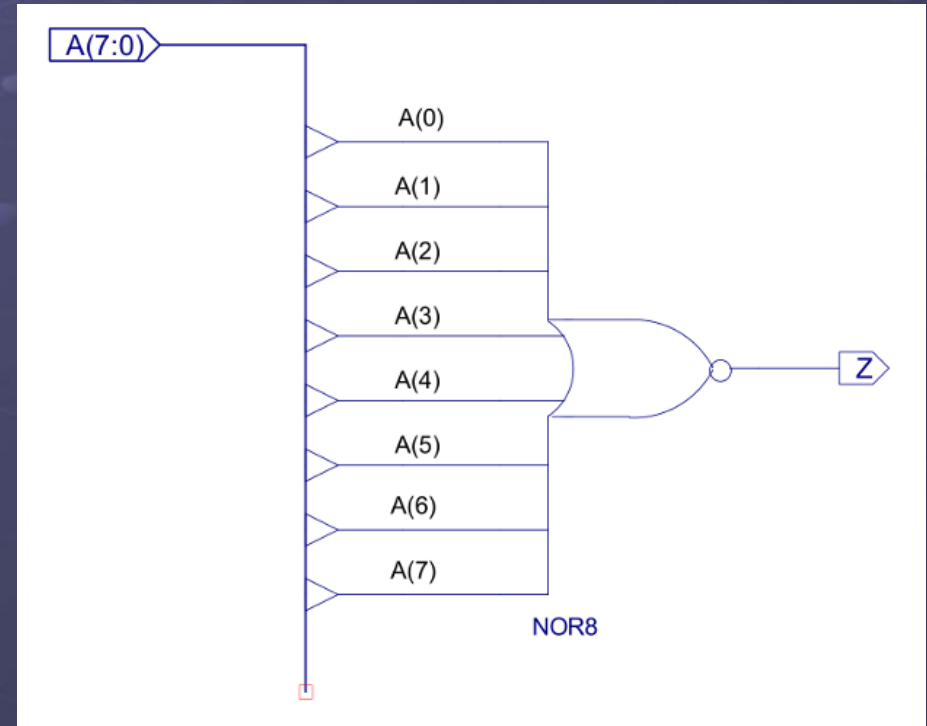



SimpleCPU_v1a

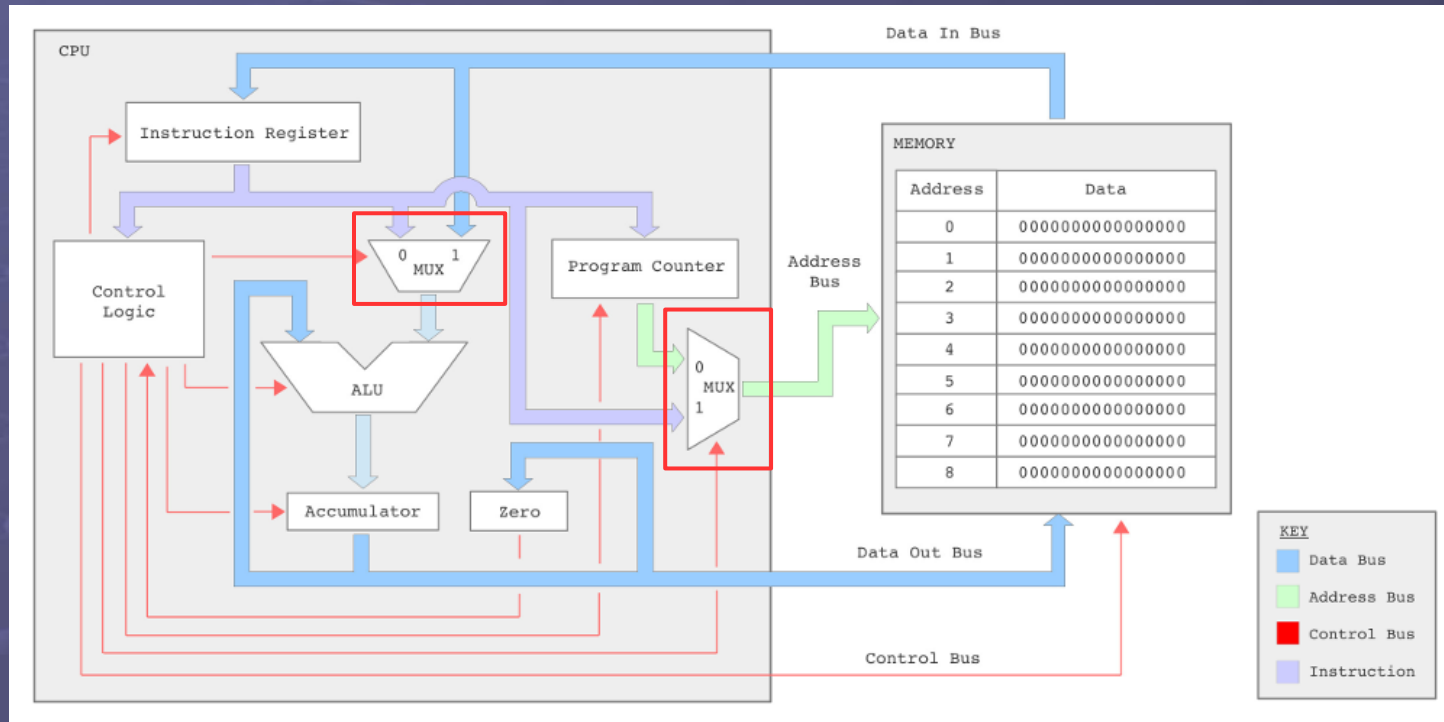

- Block diagram



- ▶ Multiplexer : a core requirement of any computer is to route / move data between functional blocks.

Multiplexers

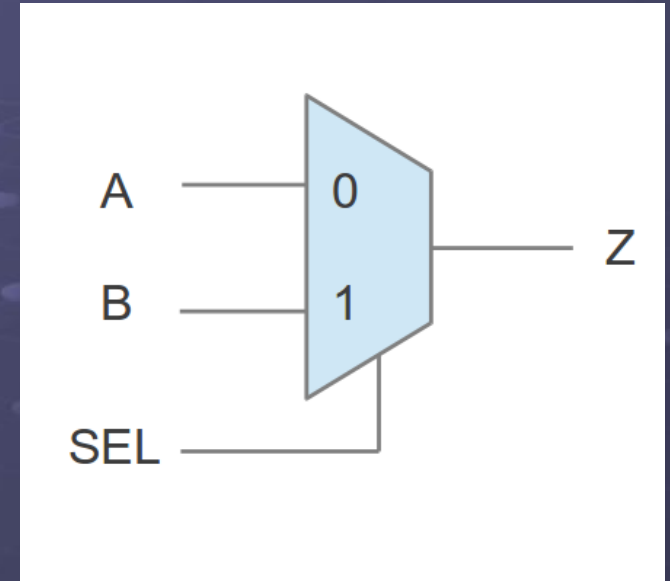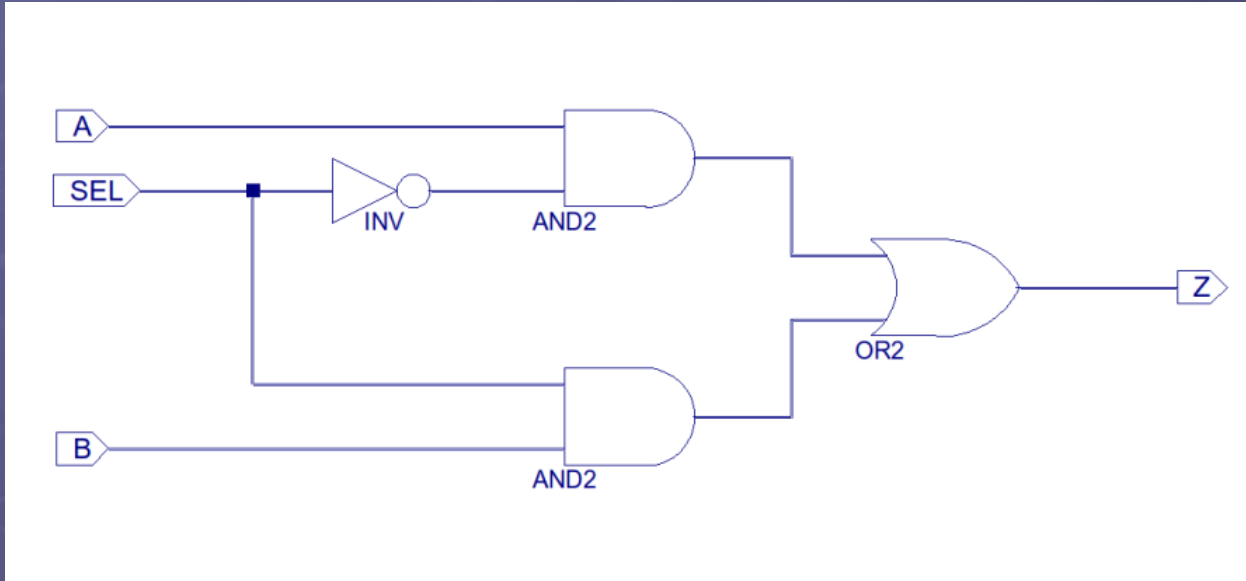



- 2:1 1bit data multiplexer (MUX)
 - ▶ Gate level implementation and Circuit Symbol
 - ▶ IF $SEL = 0$ THEN $Z = A$
 - ▶ IF $SEL = 1$ THEN $Z = B$

Multiplexers

 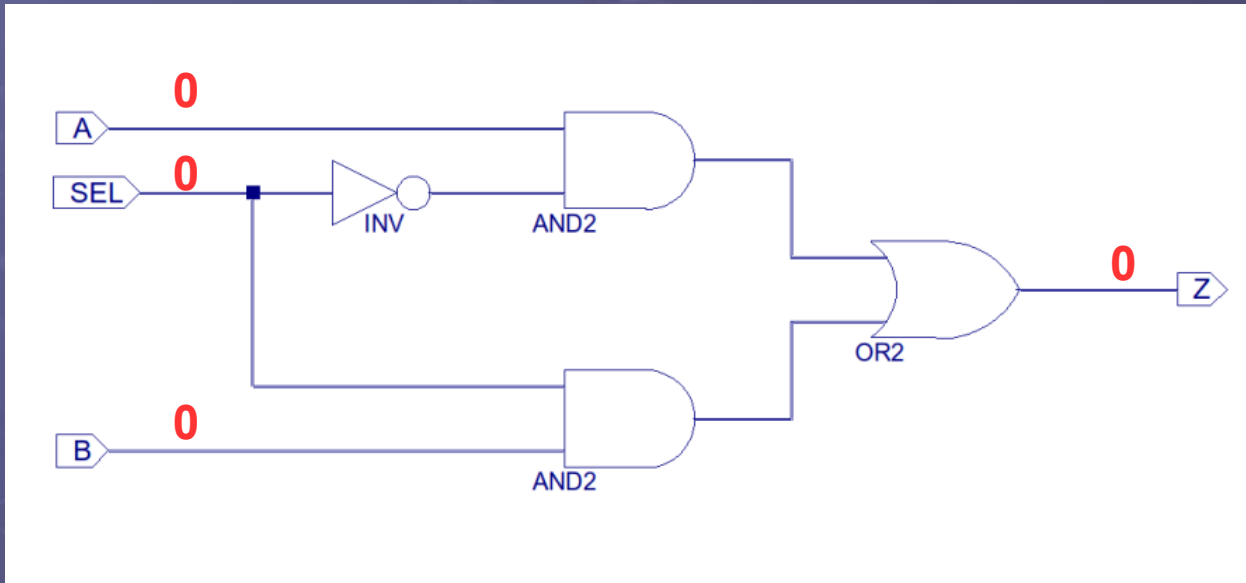



- 2:1 1bit data multiplexer (MUX)
 - ▶ Gate level implementation and Circuit Symbol
 - ▶ IF $SEL = 0$ THEN $Z = A$
 - ▶ IF $SEL = 1$ THEN $Z = B$

Multiplexers

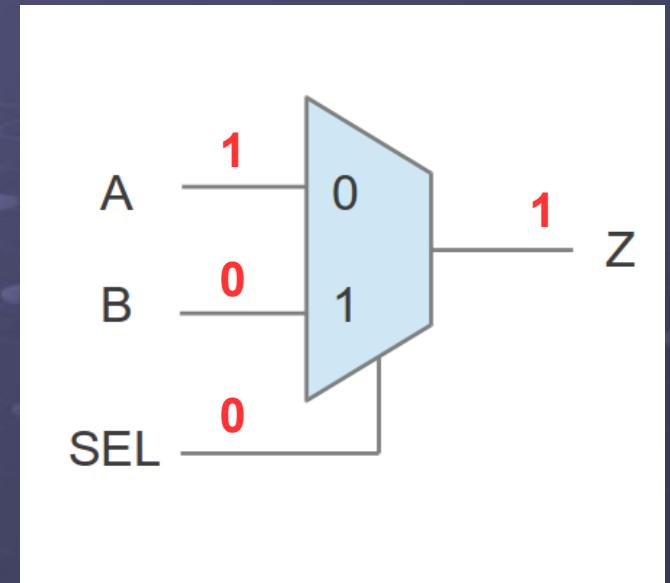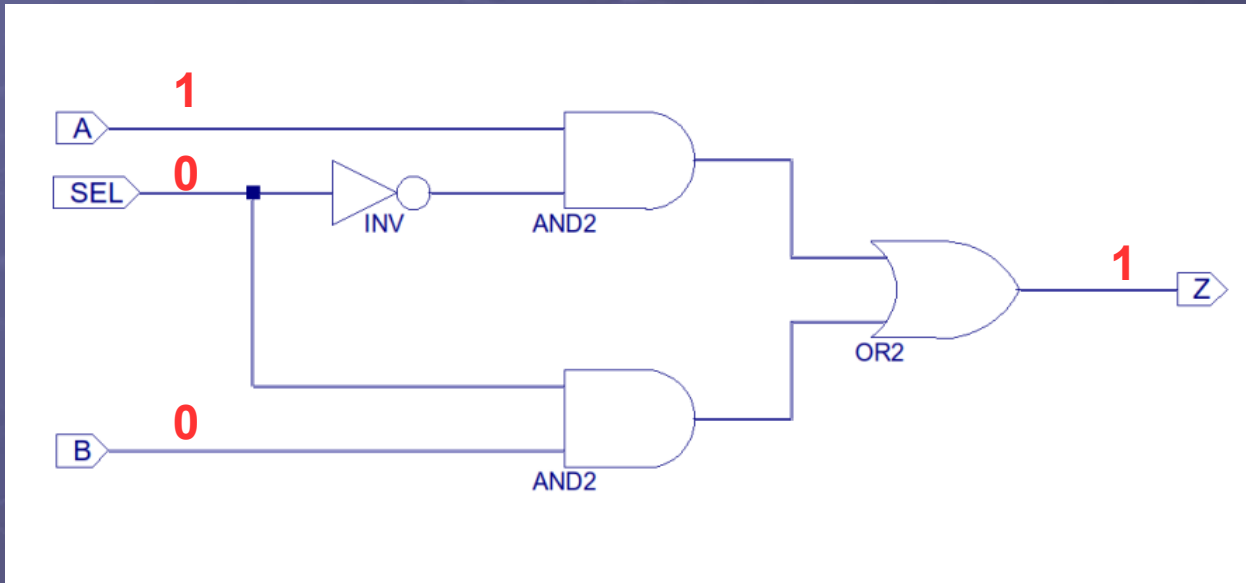



- 2:1 1bit data multiplexer (MUX)
 - ▶ Gate level implementation and Circuit Symbol
 - ▶ IF $SEL = 0$ THEN $Z = A$
 - ▶ IF $SEL = 1$ THEN $Z = B$

Multiplexers

 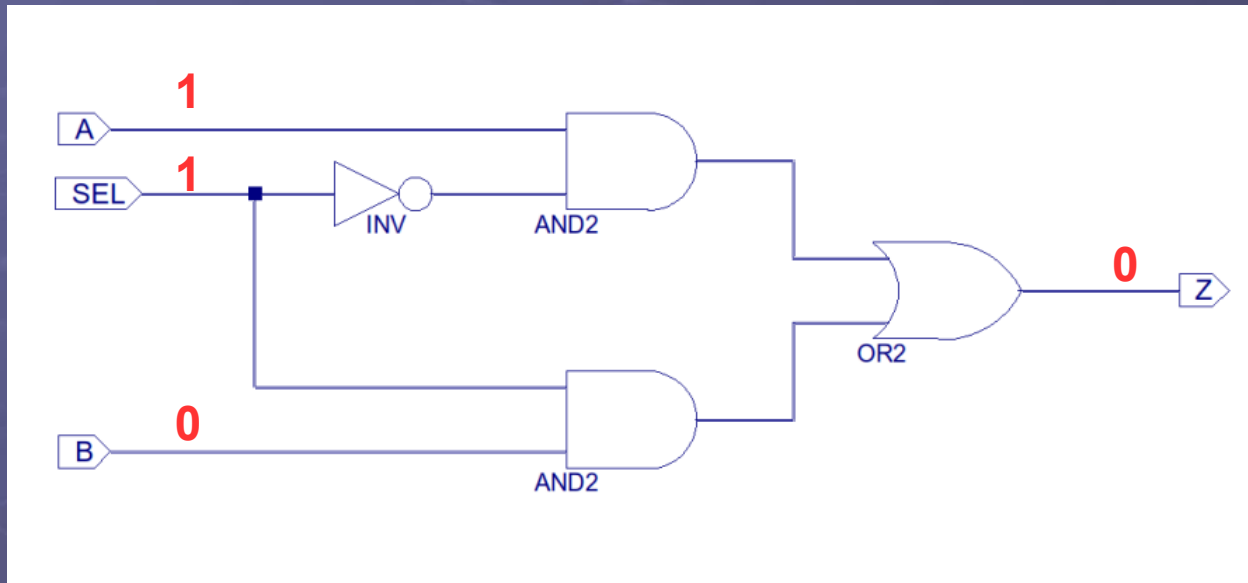


- 2:1 1bit data multiplexer (MUX)
 - ▶ Gate level implementation and Circuit Symbol
 - ▶ IF $SEL = 0$ THEN $Z = A$
 - ▶ IF $SEL = 1$ THEN $Z = B$

Multiplexers

 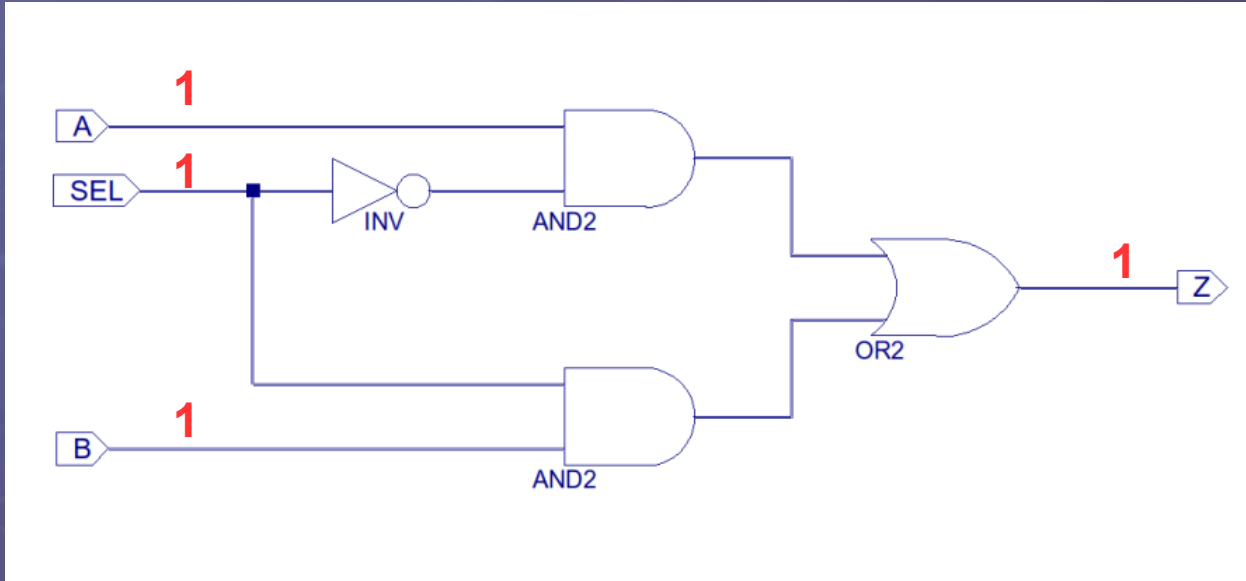



- 2:1 1bit data multiplexer (MUX)
 - ▶ Gate level implementation and Circuit Symbol
 - ▶ IF $SEL = 0$ THEN $Z = A$
 - ▶ IF $SEL = 1$ THEN $Z = B$

SimpleCPU_v1a

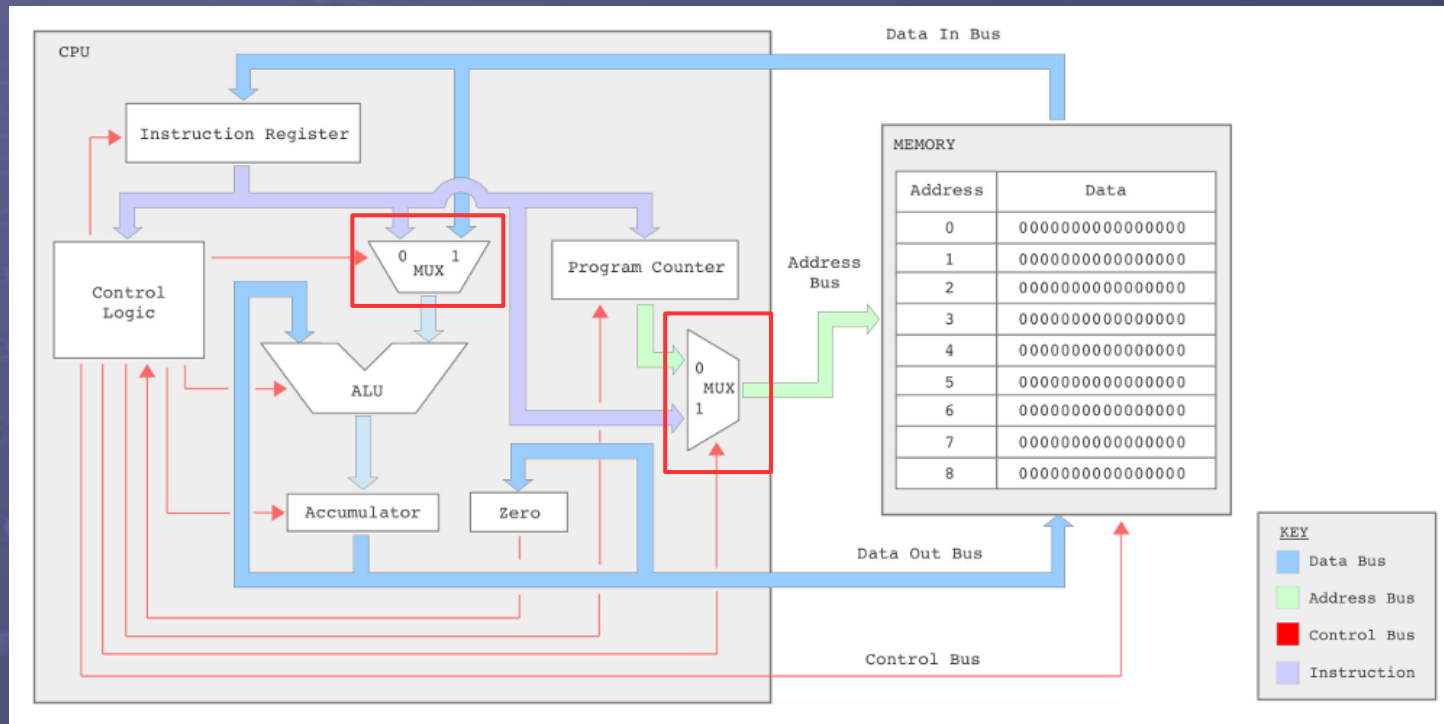


- Problem : the two highlighted multiplexers need to select between two 8 bit values.
 - ▶ May also need to select between more than two input sources.

Multiplexers

 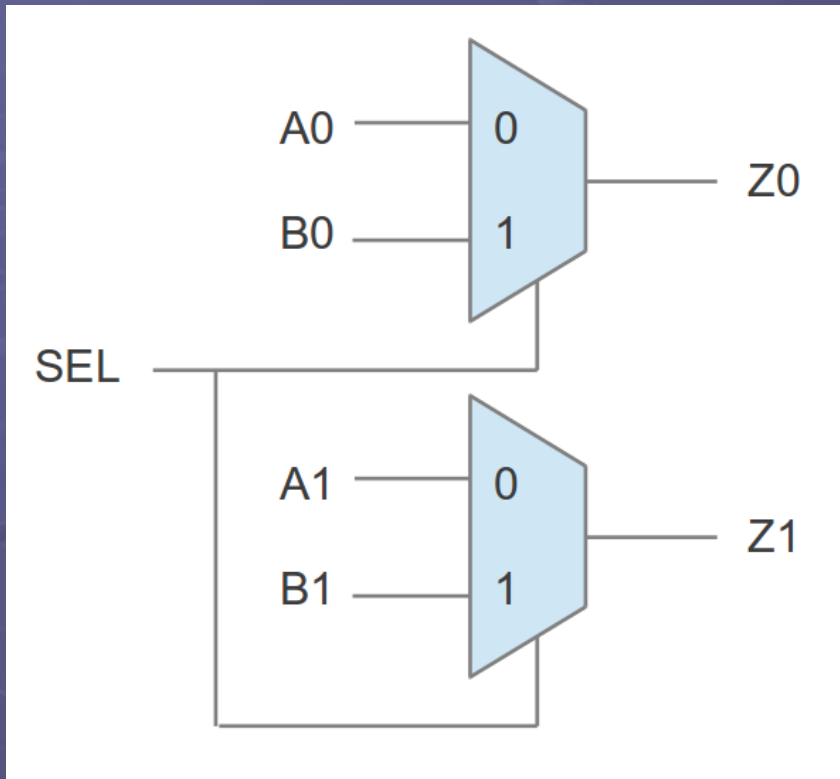


- 2:1 x 2bit MUX: Parallel MUX to increase width
- 3:1 x 1bit MUX: Serial MUX to increase inputs

Multiplexers

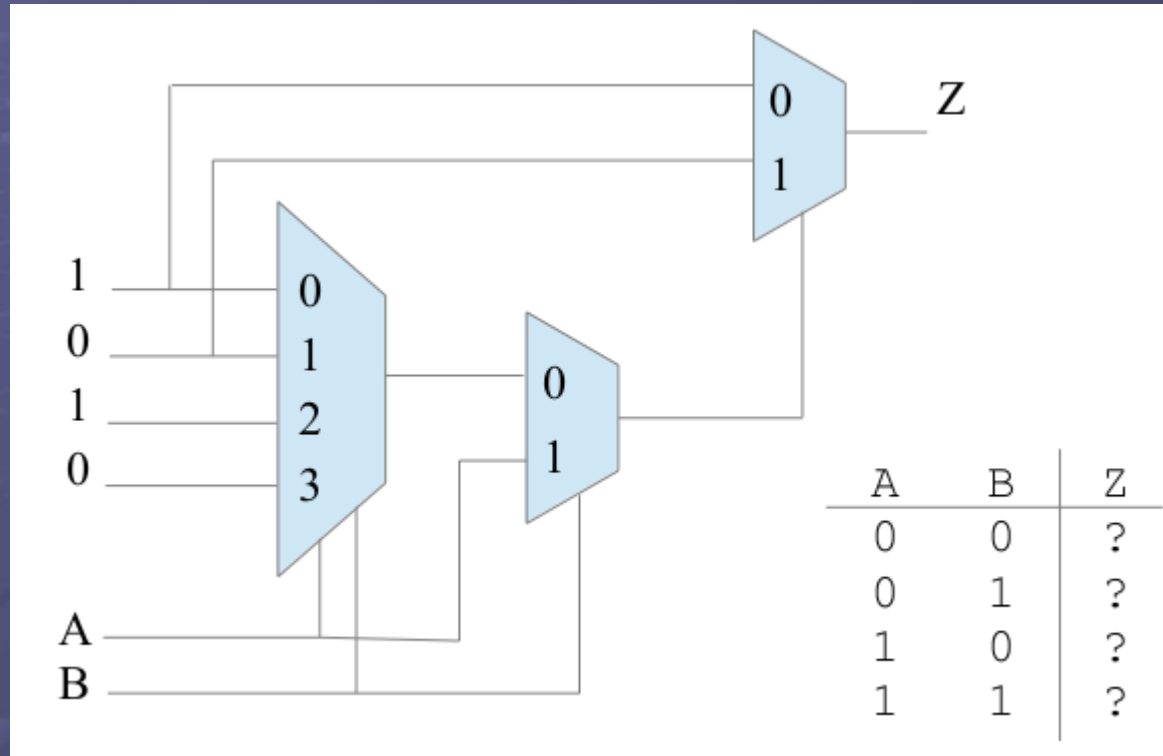



- Quick quiz: complete the truth table
 - ▶ Bonus question : what two logic gates can be used to implement this circuit?

Example : MUX_2.zip

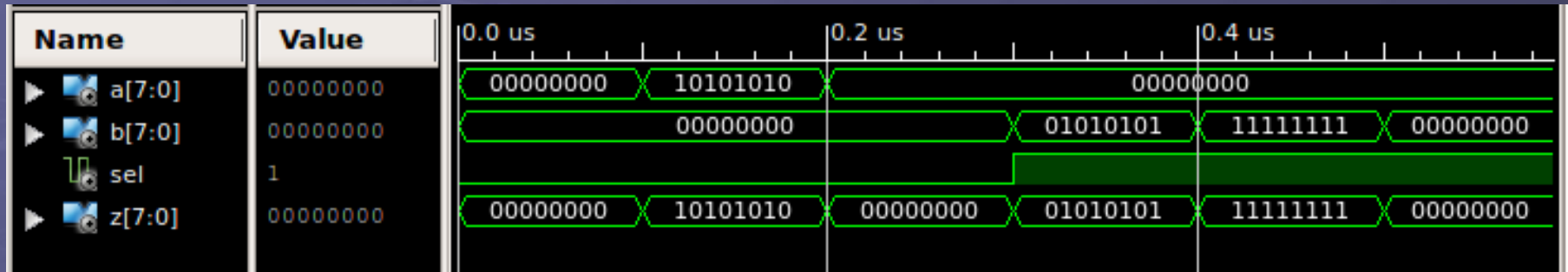


- Simulation

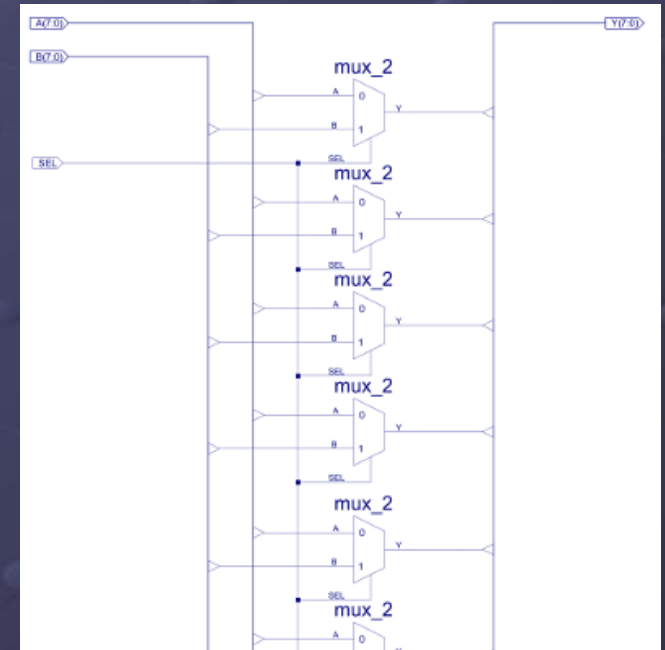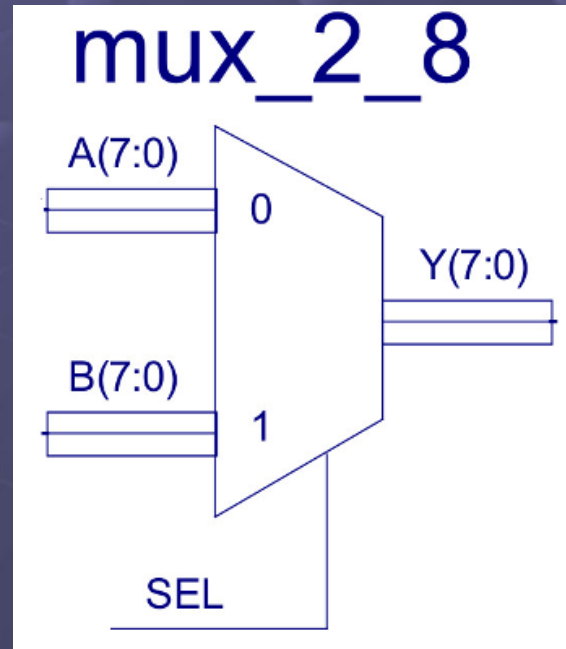- ▶ MUX_2_8 : a two input 8 bit multiplexer
- ▶ MUX_4_8 : a four input 8 bit multiplexer



SimpleCPU_v1a

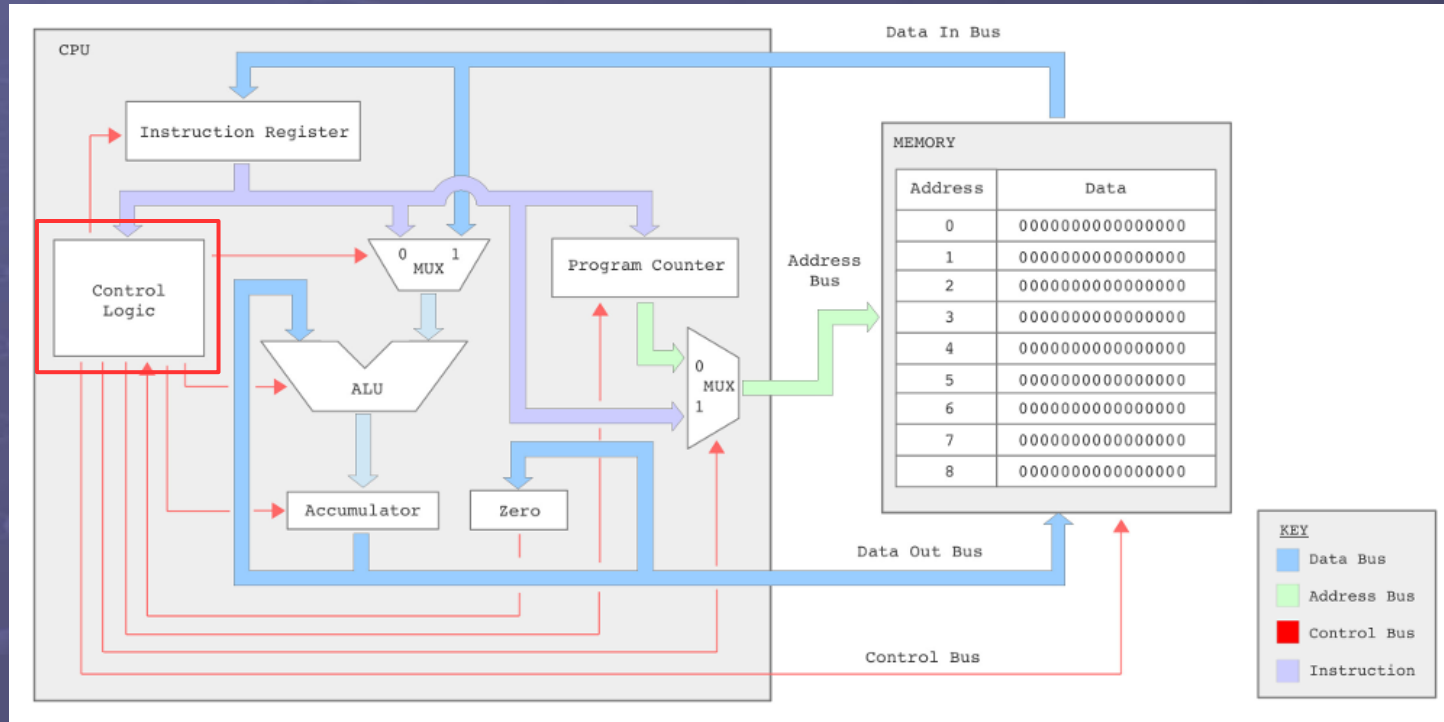

- Block diagram


- ▶ Encoders / Decoders : within the processor information is stored using a range of binary representations.

Binary encoding

<i>Decimal</i>	<i>Binary</i>	<i>BCD</i>	<i>One-hot</i>
0	0000 0000	0000 0000	0000 0000 0000 0001
1	0000 0001	0000 0001	0000 0000 0000 0010
2	0000 0010	0000 0010	0000 0000 0000 0100
3	0000 0011	0000 0011	0000 0000 0000 1000
4	0000 0100	0000 0100	0000 0000 0001 0000
5	0000 0101	0000 0101	0000 0000 0010 0000
6	0000 0110	0000 0110	0000 0000 0100 0000
7	0000 0111	0000 0111	0000 0000 1000 0000
8	0000 1000	0000 1000	0000 0001 0000 0000
9	0000 1001	0000 1001	0000 0010 0000 0000
10	0000 1010	0001 0000	0000 0100 0000 0000
11	0000 1011	0001 0001	0000 1000 0000 0000
12	0000 1100	0001 0010	0001 0000 0000 0000
13	0000 1101	0001 0011	0010 0000 0000 0000
14	0000 1110	0001 0100	0100 0000 0000 0000
15	0000 1111	0001 0101	1000 0000 0000 0000


- Alternative binary representations : Binary Coded Decimal (BCD) and One-hot encoding.

Encoder / Decoder

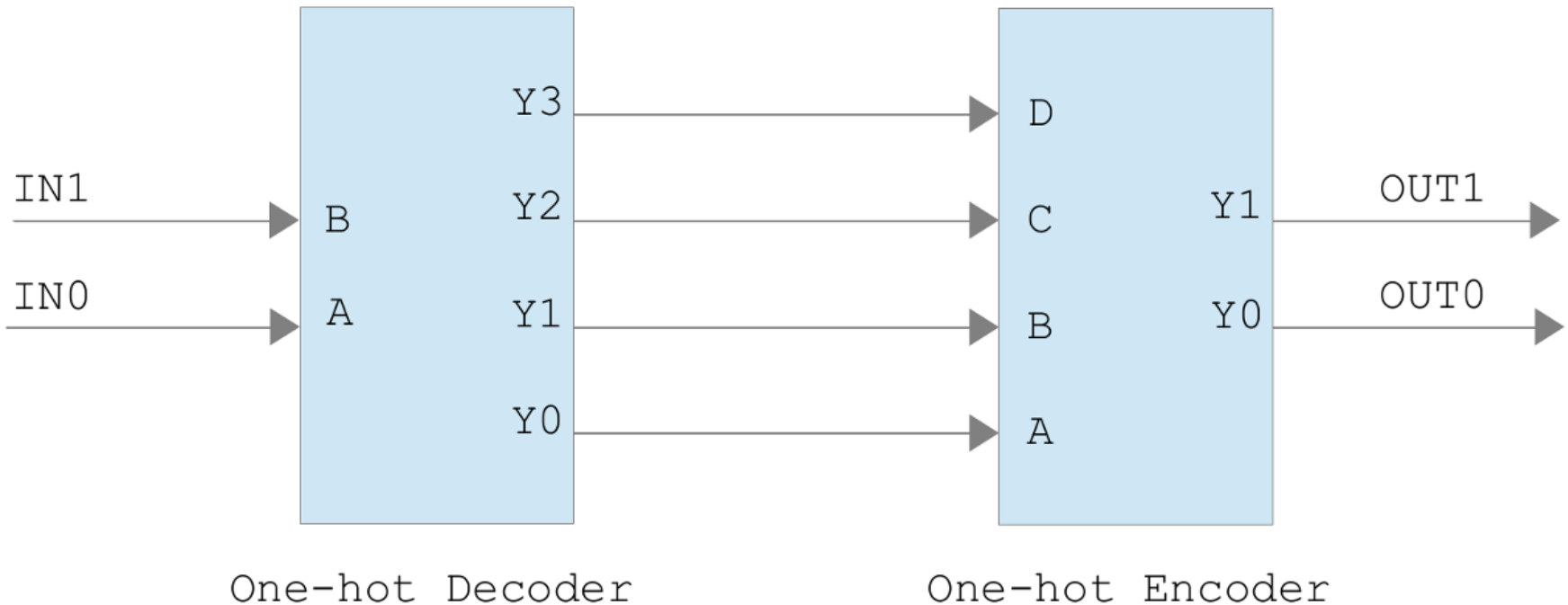


- A two bit binary to One-hot encoder and decoder

Encoder / Decoder

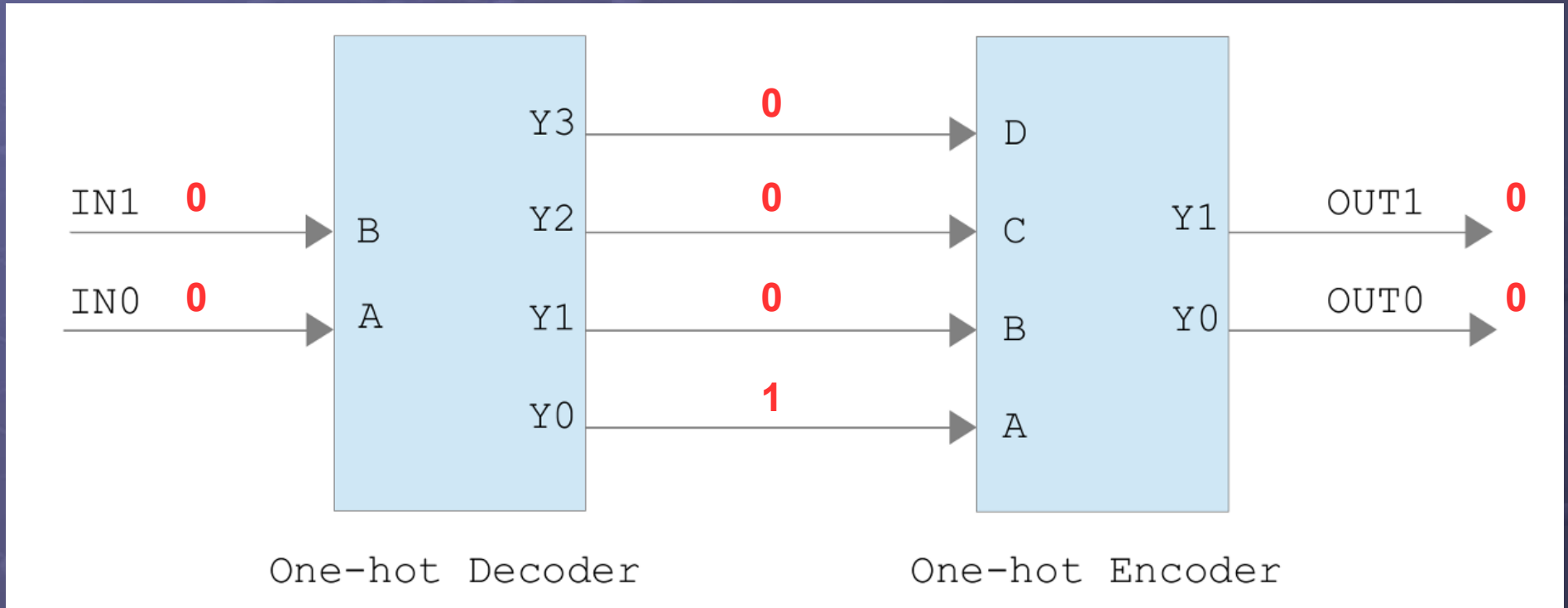


- A two bit binary to One-hot encoder and decoder

Encoder / Decoder

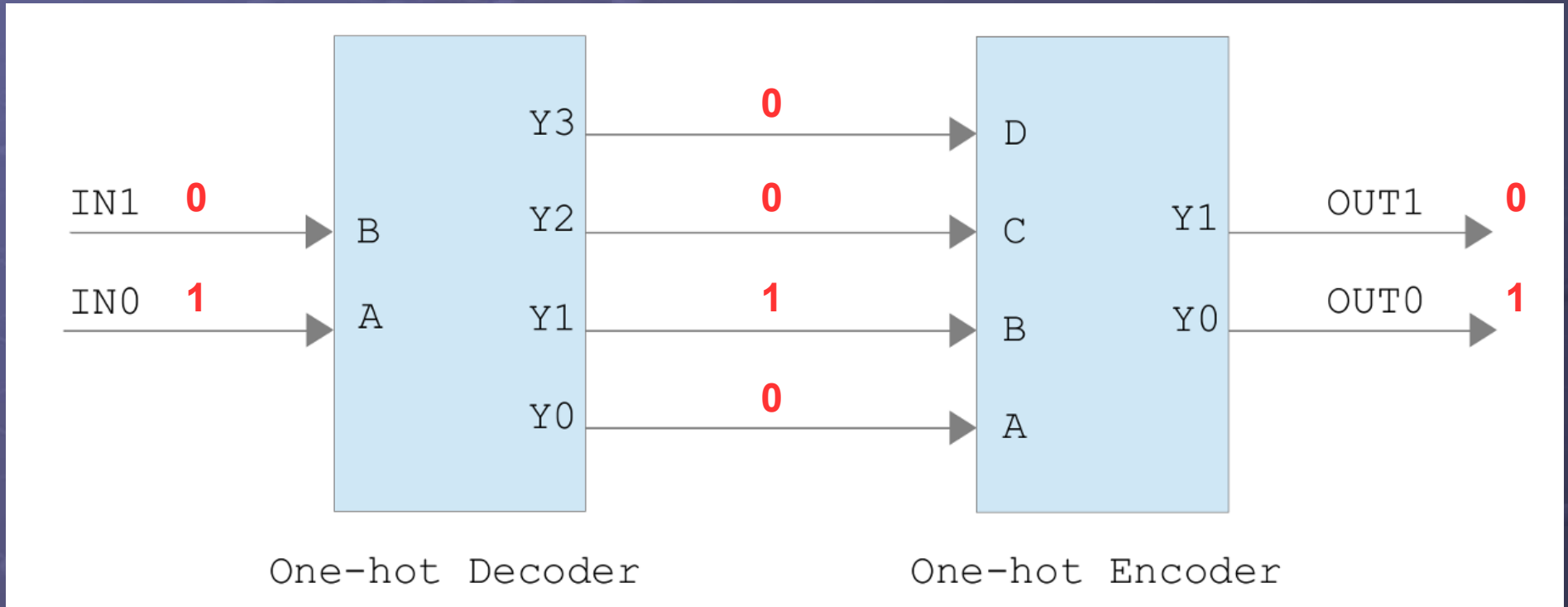


- A two bit binary to One-hot encoder and decoder

Encoder / Decoder

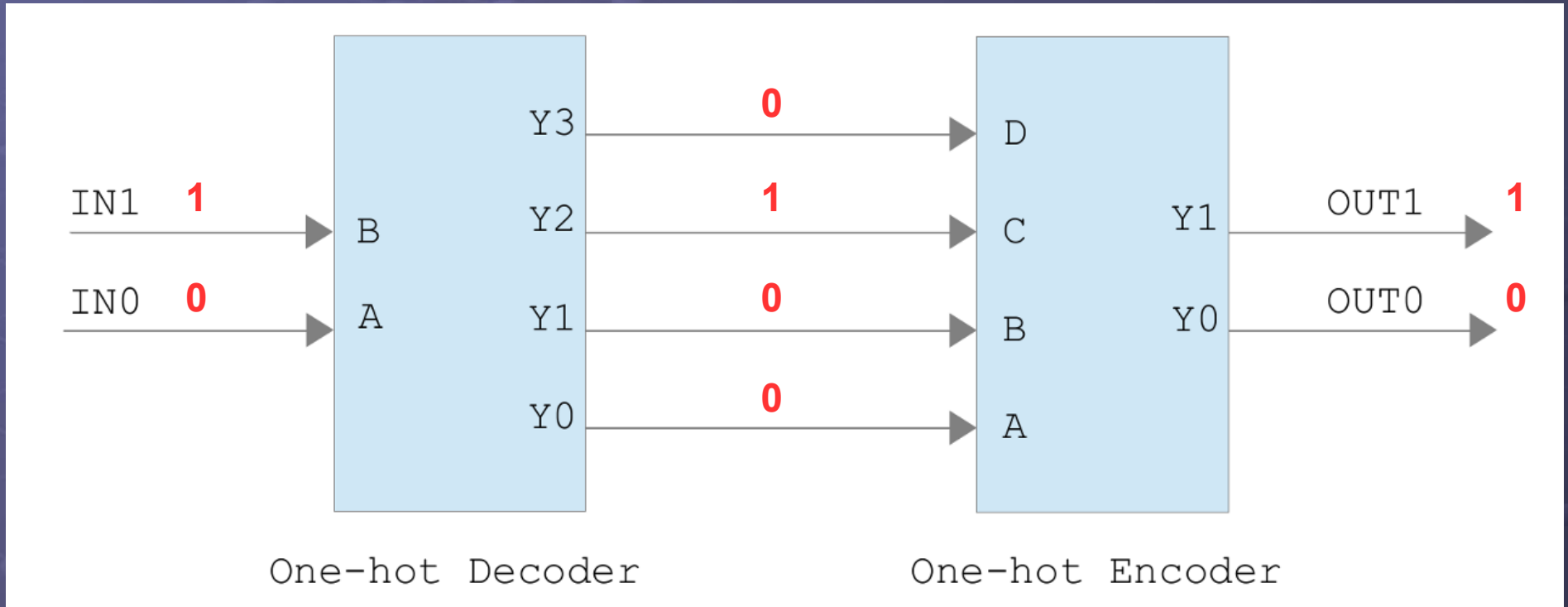



- A two bit binary to One-hot encoder and decoder

Encoder / Decoder

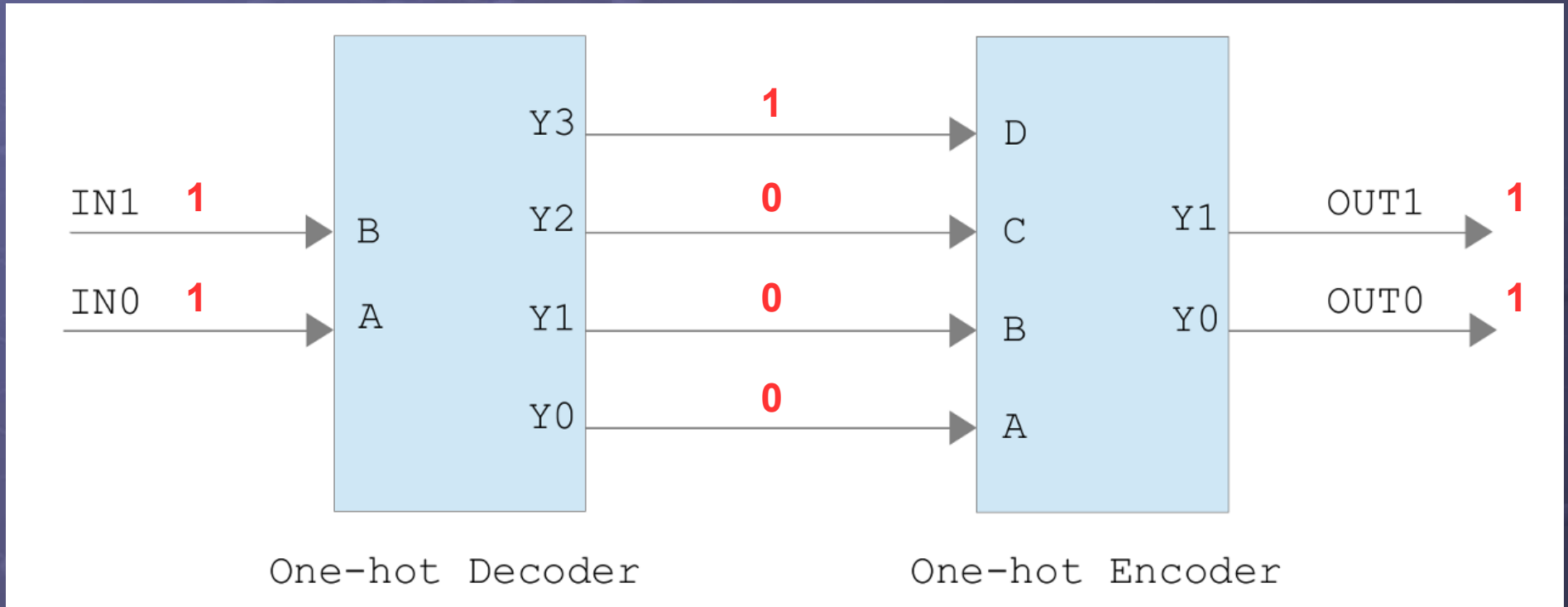

- A two bit binary to One-hot encoder and decoder



Decoder

 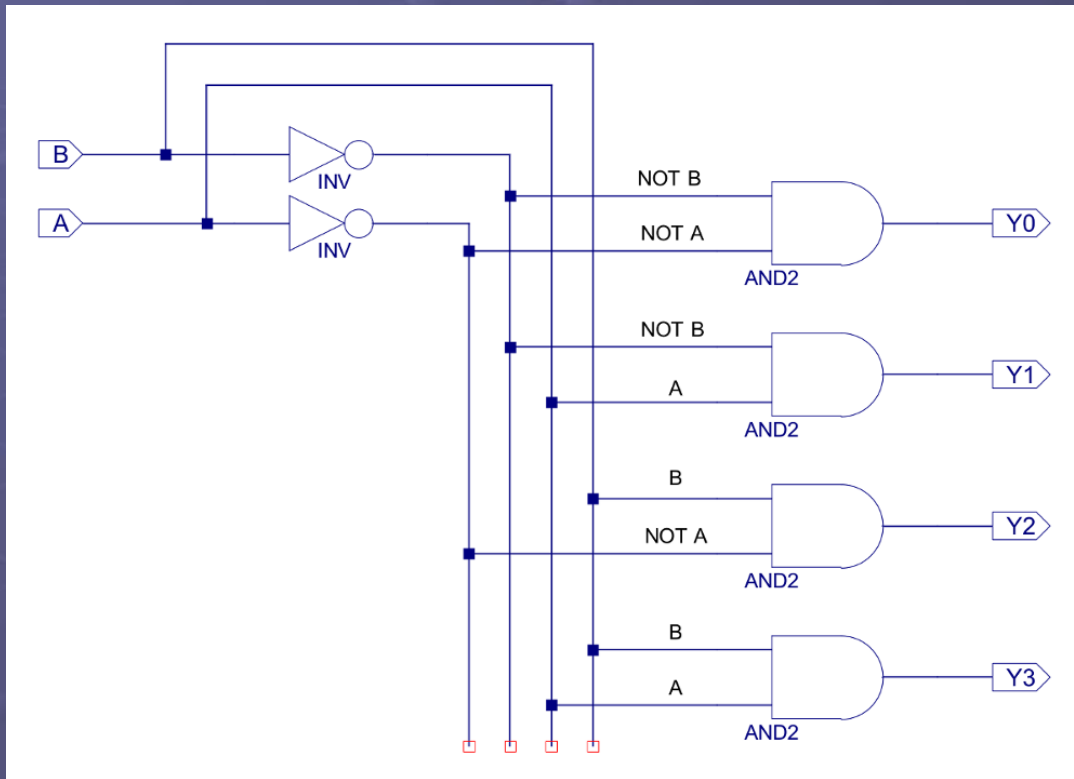

- 2bit Binary to One-hot decoder

B	A	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1



Decoder

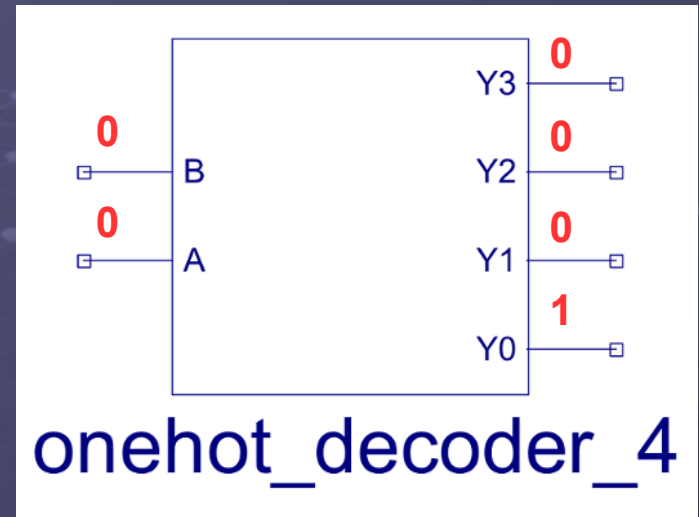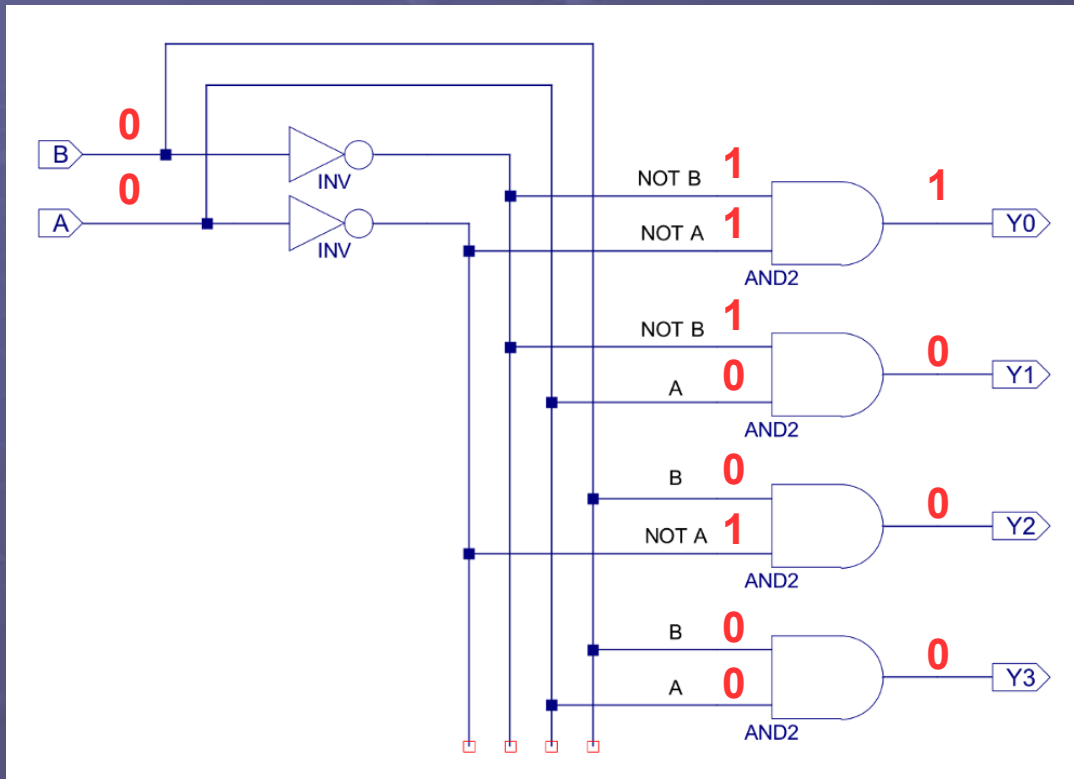

- 2bit Binary to One-hot decoder

B	A	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1



Decoder

 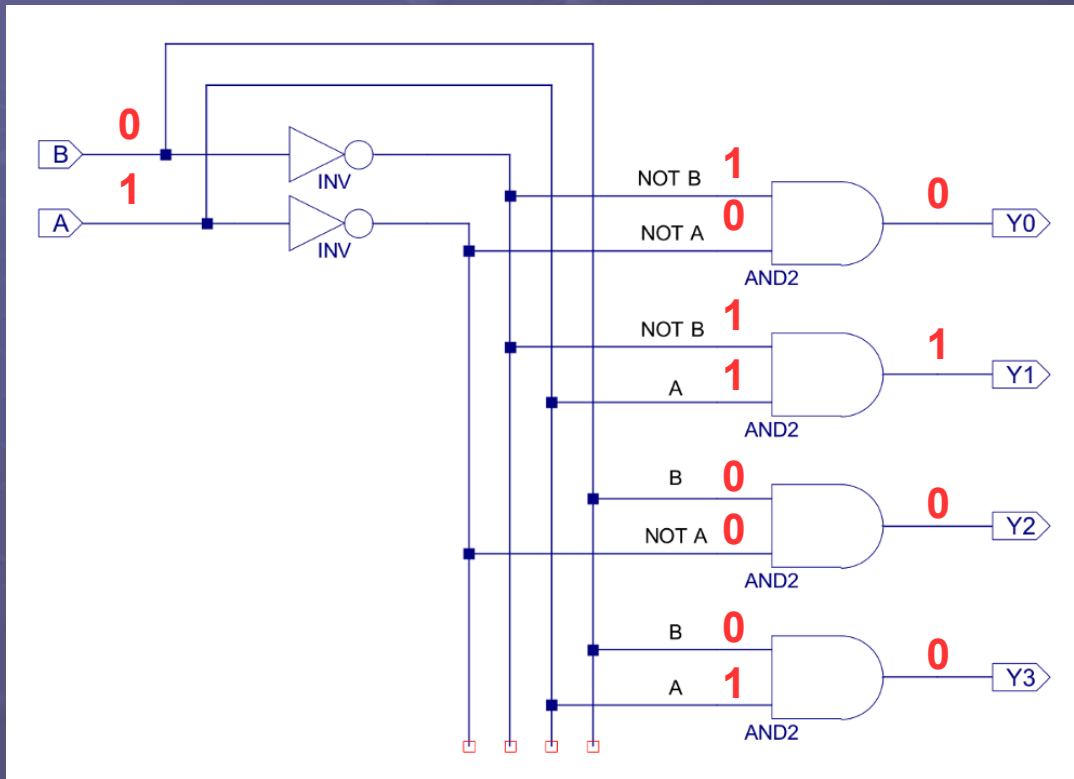

- 2bit Binary to One-hot decoder

B	A	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1



Decoder

 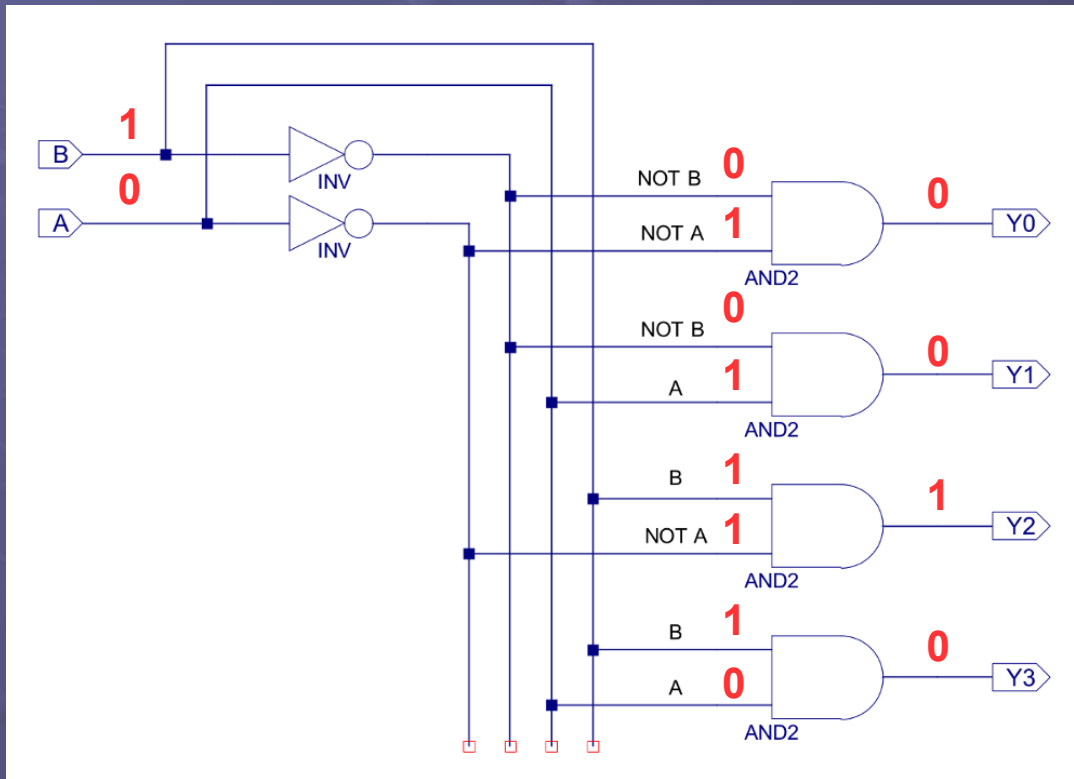

- 2bit Binary to One-hot decoder

B	A	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Decoder

 
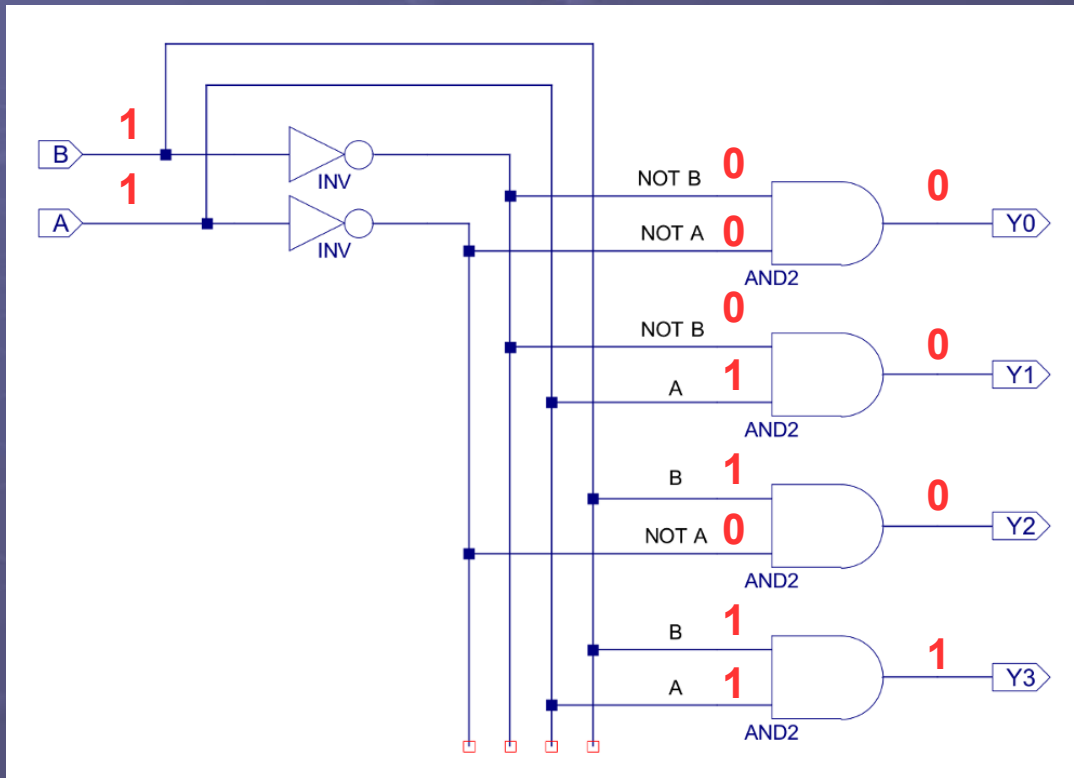


onehot_decoder_4

- 2bit Binary to One-hot decoder

B	A	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1



Encoder

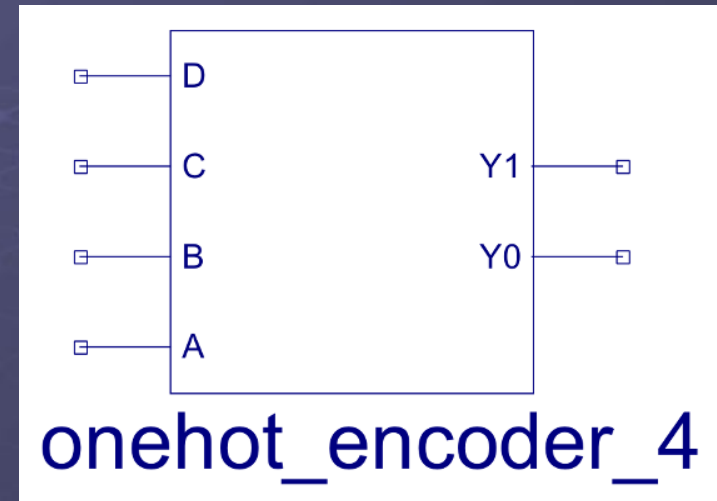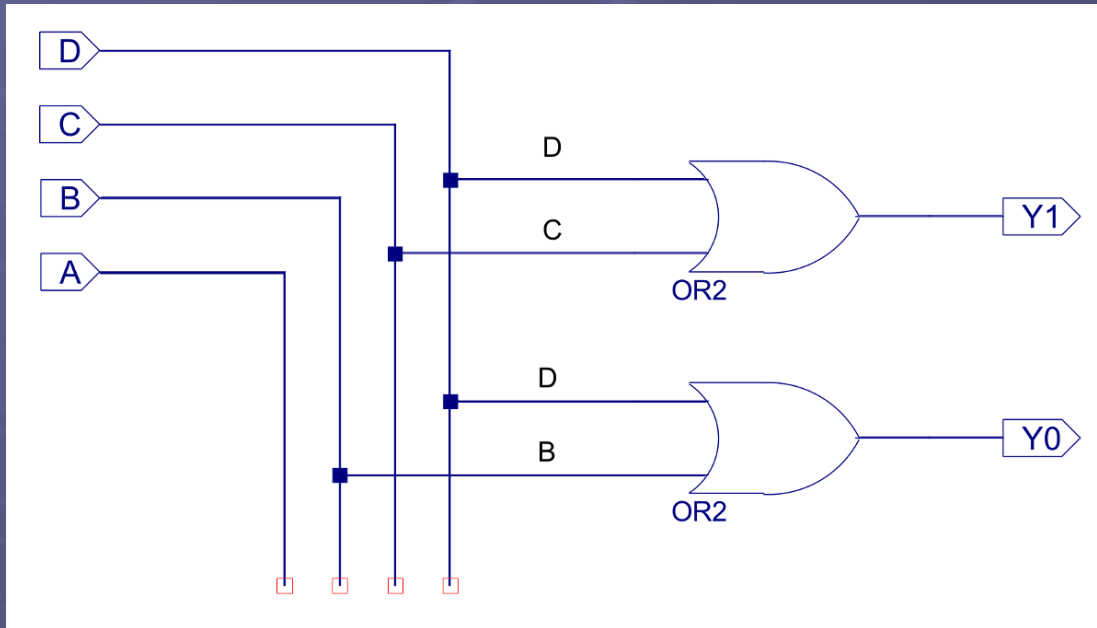

- 2bit One-hot to Binary encoder
 - ▶ One-hot representation simplifies logic design i.e. only 1 bit is ever set.
 - ◆ Identify when output is a logic 1 then join active inputs with OR gates.

D	C	B	A	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Encoder

 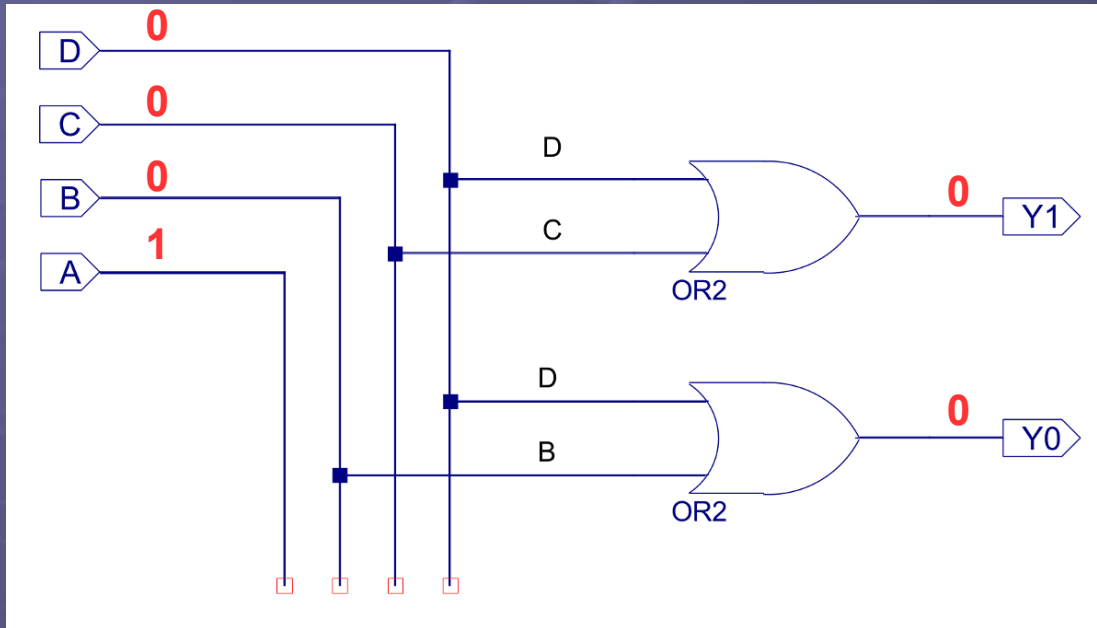



- 2bit One-hot to Binary encoder

- ▶ One-hot representation simplifies logic design i.e. only 1 bit is ever set.

- ◆ Identify when output is a logic 1 then join active inputs with OR gates.

D	C	B	A	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Encoder

 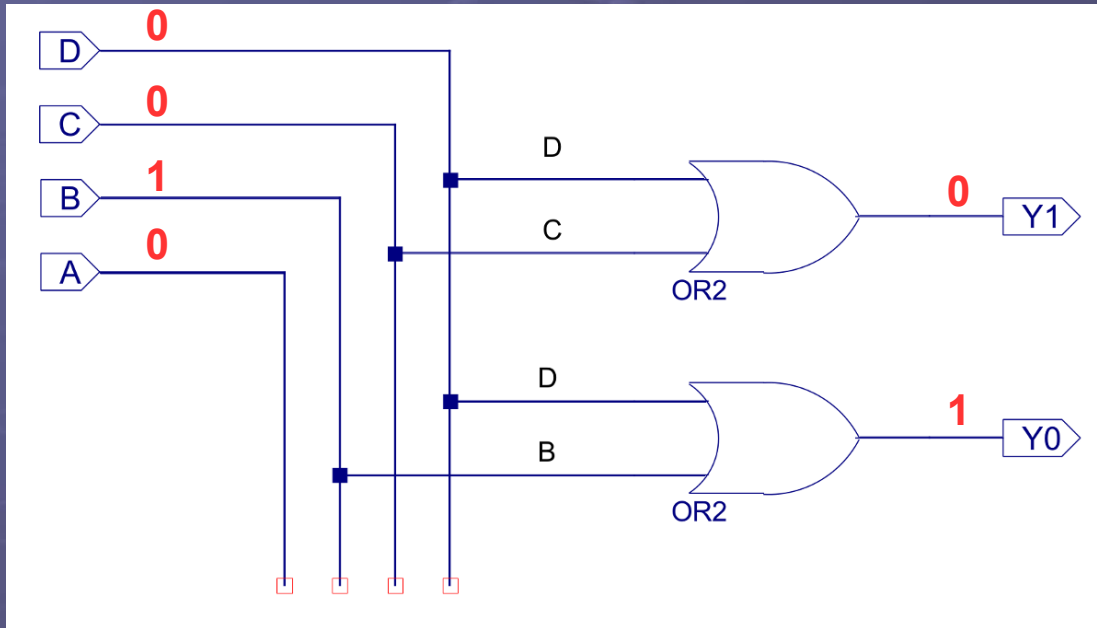



- 2bit One-hot to Binary encoder

- ▶ One-hot representation simplifies logic design i.e. only 1 bit is ever set.

- ◆ Identify when output is a logic 1 then join active inputs with OR gates.

D	C	B	A	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1



Encoder

 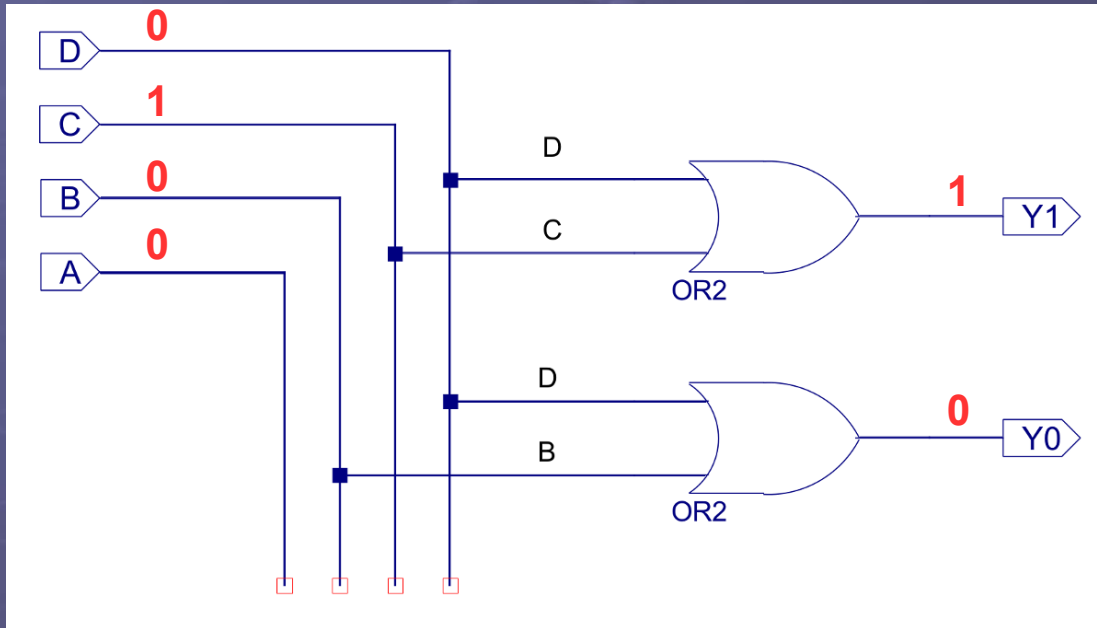

- 2bit One-hot to Binary encoder
 - ▶ One-hot representation simplifies logic design i.e. only 1 bit is ever set.
 - ◆ Identify when output is a logic 1 then join active inputs with OR gates.

D	C	B	A	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Encoder

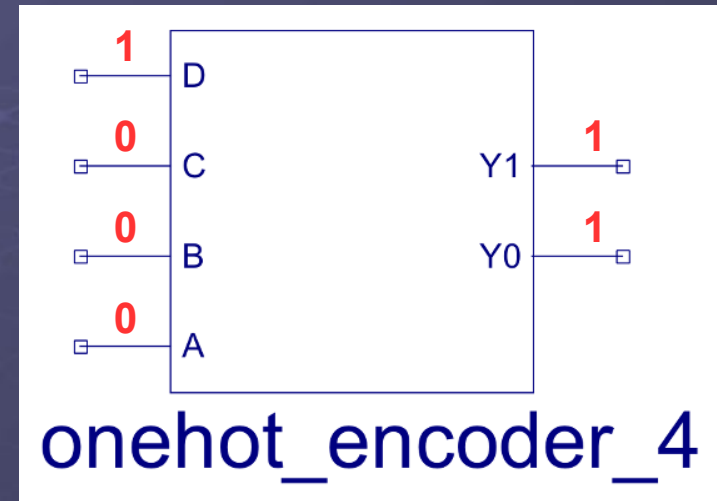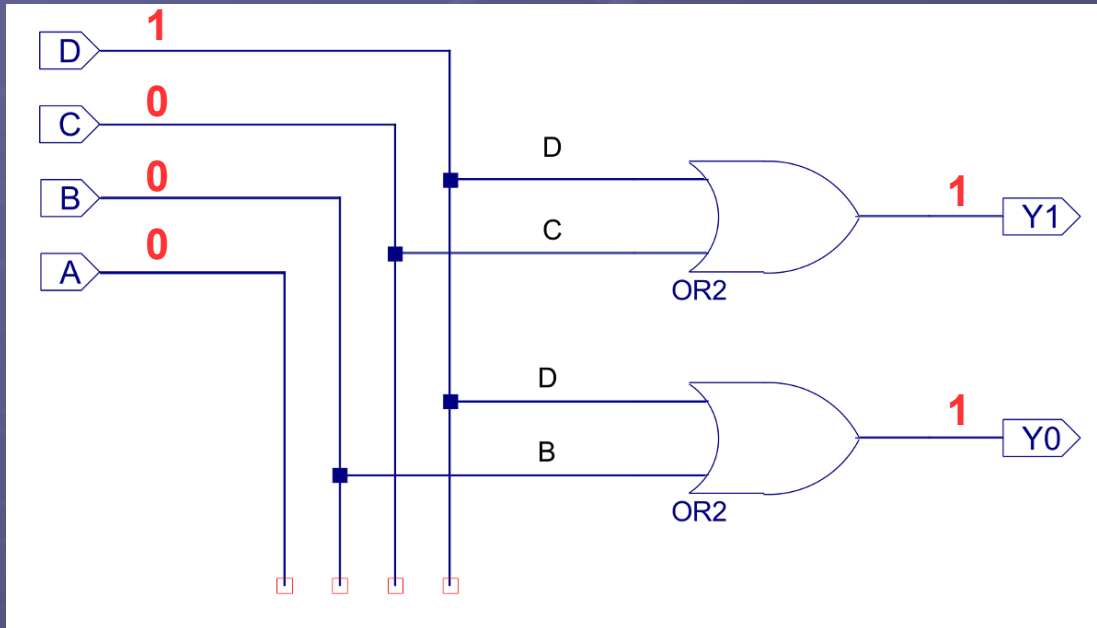

- 2bit One-hot to Binary encoder

- ▶ One-hot representation simplifies logic design i.e. only 1 bit is ever set.

- ◆ Identify when output is a logic 1 then join active inputs with OR gates.

D	C	B	A	Y1	Y0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Encoder / Decoder

Which of the following is a valid one-hot value?


A) 00000000 B) 01000000 C) 10000010

An instruction is represented within a computer by a two bit binary number:

0 1 = Add 0 0 = Subtract


1 0 = Multiply 1 1 = Divide

 This two bit code is decoded using the `onehot_decoder_4` component to produce control signals `S0`, `S1`, `S2` and `S3`. Complete the truth table below, identifying what instruction is being processed.




- Quick quizzz


Example : onehot_encoder.zip

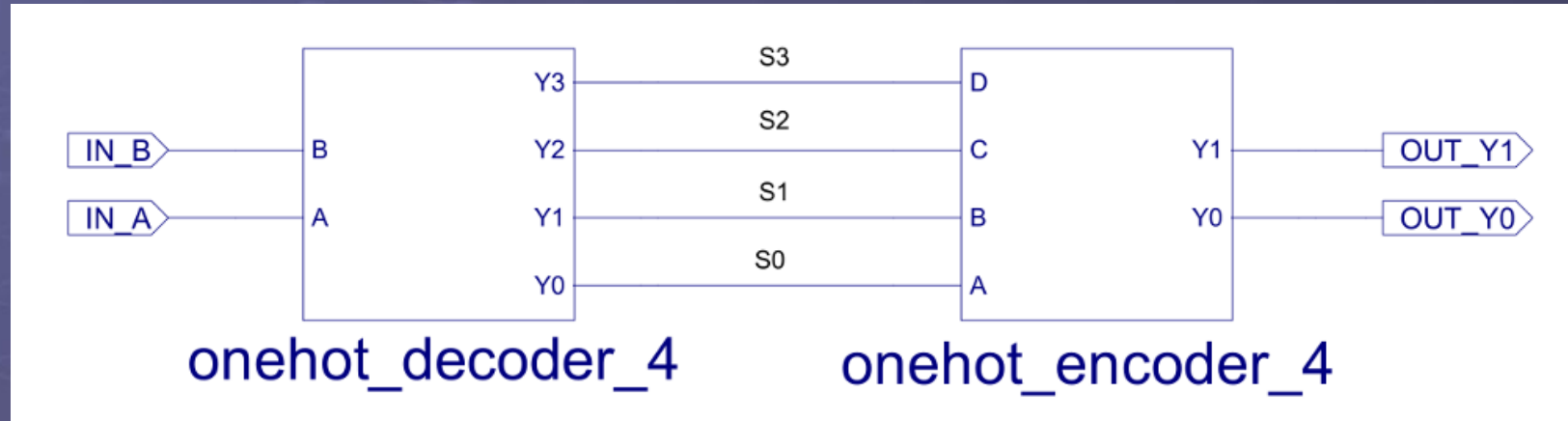

 - Simulation
 - ▶ 2 bit input A, B
 - ▶ 2 bit output Y1, Y0



SimpleCPU_v1a

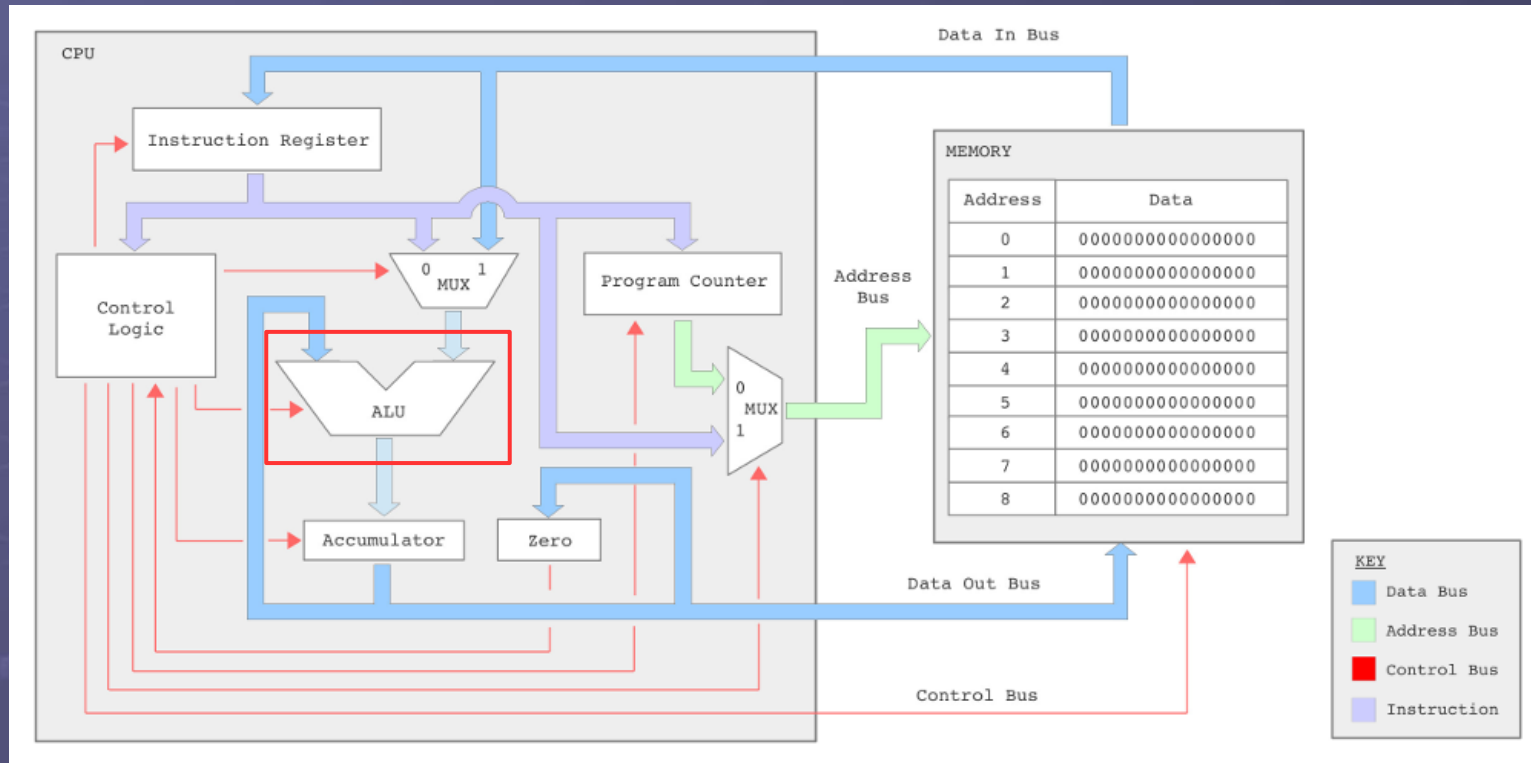

- Block diagram

- ▶ ALU : a core requirement of any computer is to process data i.e. the Arithmetic and Logic unit, the ADDER the heart of any CPU.

Key skills : working in base 2

$$\begin{array}{r} 0110101 \\ +0011100 \\ \hline 1 \\ \hline \end{array} \qquad \begin{array}{r} 53 \\ +28 \\ \hline \\ \hline \end{array}$$

- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer

Key skills : working in base 2

$$\begin{array}{r} 0110101 \\ +0011100 \\ \hline 01 \\ \hline \end{array}$$
$$\begin{array}{r} 53 \\ +28 \\ \hline \\ \hline \end{array}$$

- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer

Key skills : working in base 2

$$\begin{array}{r} 0110101 \\ +0011100 \\ \hline 001 \\ \hline 1 \end{array}$$
$$\begin{array}{r} 53 \\ +28 \\ \hline \hline \end{array}$$

- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer

Key skills : working in base 2

$$\begin{array}{r} 0110101 \\ +0011100 \\ \hline 0001 \\ \hline 11 \end{array} \qquad \begin{array}{r} 53 \\ +28 \\ \hline \\ \hline \end{array}$$

- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer

Key skills : working in base 2

$$\begin{array}{r} 0110101 \\ +0011100 \\ \hline 10001 \\ \hline 111 \end{array} \qquad \begin{array}{r} 53 \\ +28 \\ \hline \\ \hline \end{array}$$

- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer

Key skills : working in base 2

$$\begin{array}{r} 0110101 \\ +0011100 \\ \hline 010001 \\ \hline 1111 \end{array} \qquad \begin{array}{r} 53 \\ +28 \\ \hline \\ \hline \end{array}$$


- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer

Key skills : working in base 2

$$\begin{array}{r} 0110101 \\ +0011100 \\ \hline 1010001 \\ \hline 1111 \end{array} \qquad \begin{array}{r} 53 \\ +28 \\ \hline 81 \\ \hline \end{array}$$

- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer


Binary addition

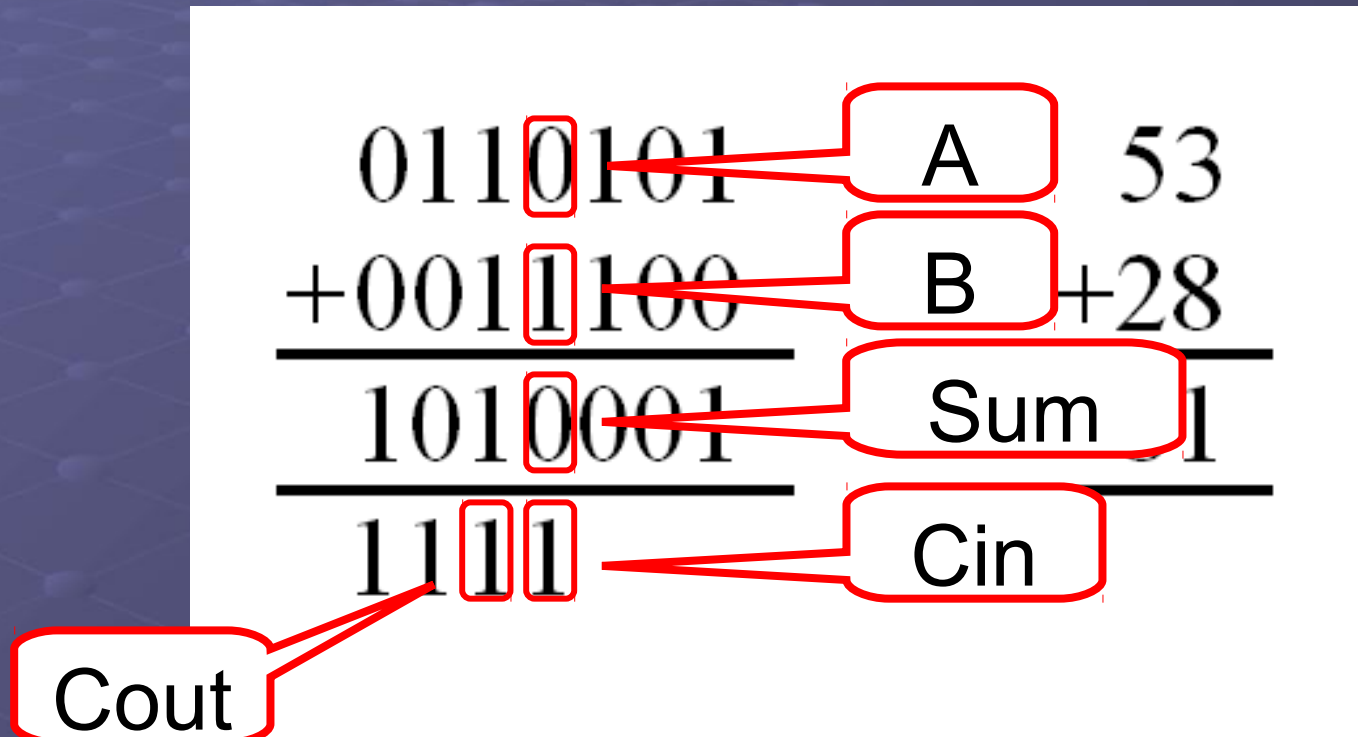


- Adding two binary numbers : 53 + 28
 - ▶ Positive, integer

Binary addition

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


A	B	Cin	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

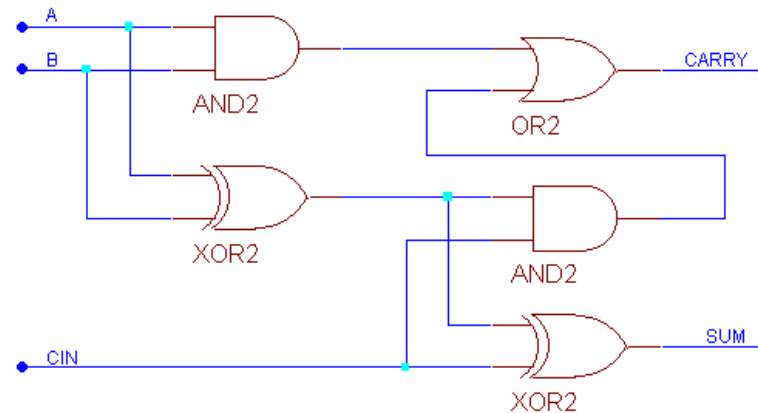


- Half and full adder
 - ▶ Basic components can be combined into larger circuits

Binary addition

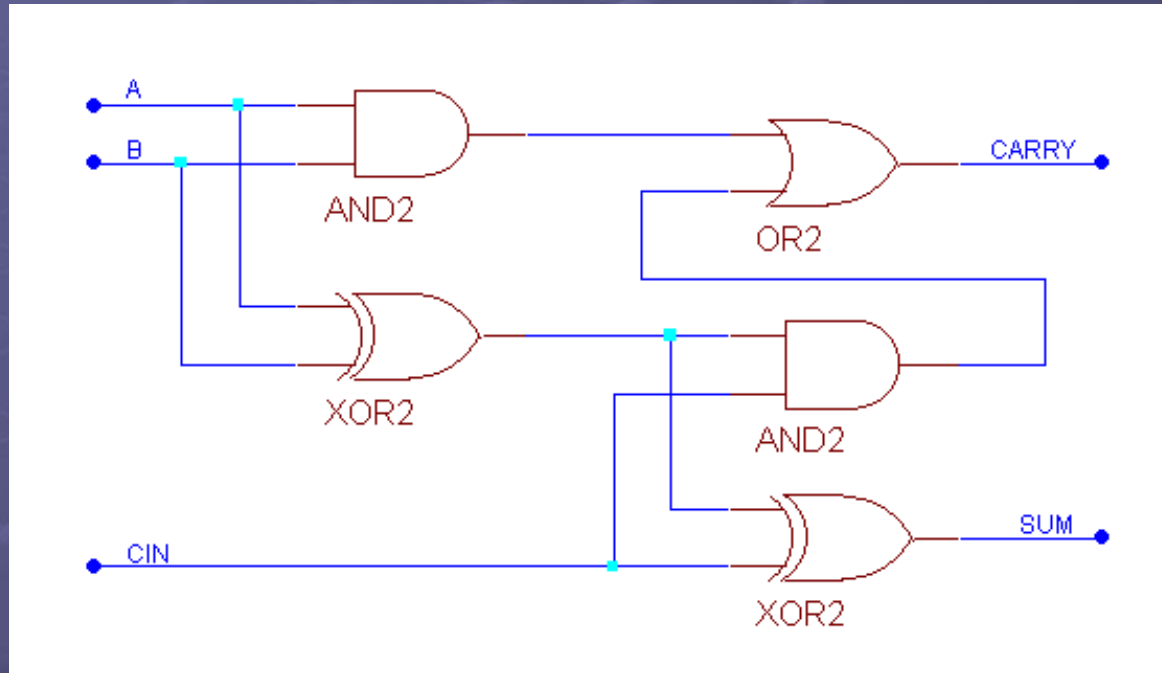

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

 

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1




A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0




- Full Adder operation

Binary addition

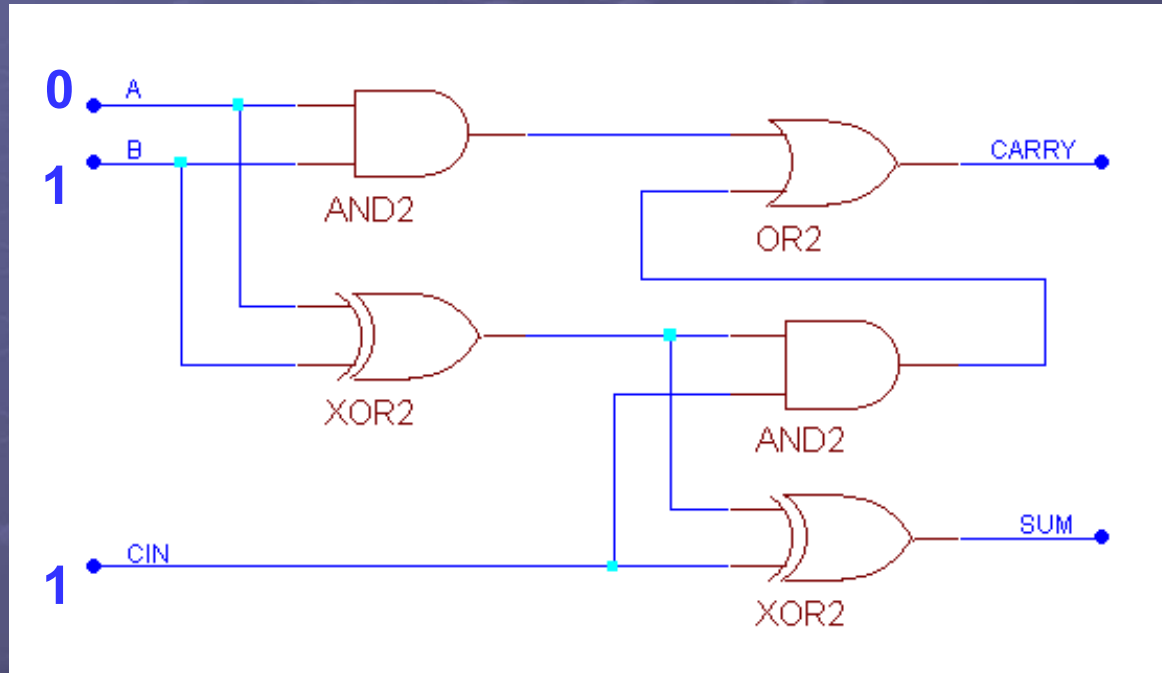

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

 

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1




A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0



- Full Adder operation
 - ▶ A=0, B=1, C=1

Binary addition

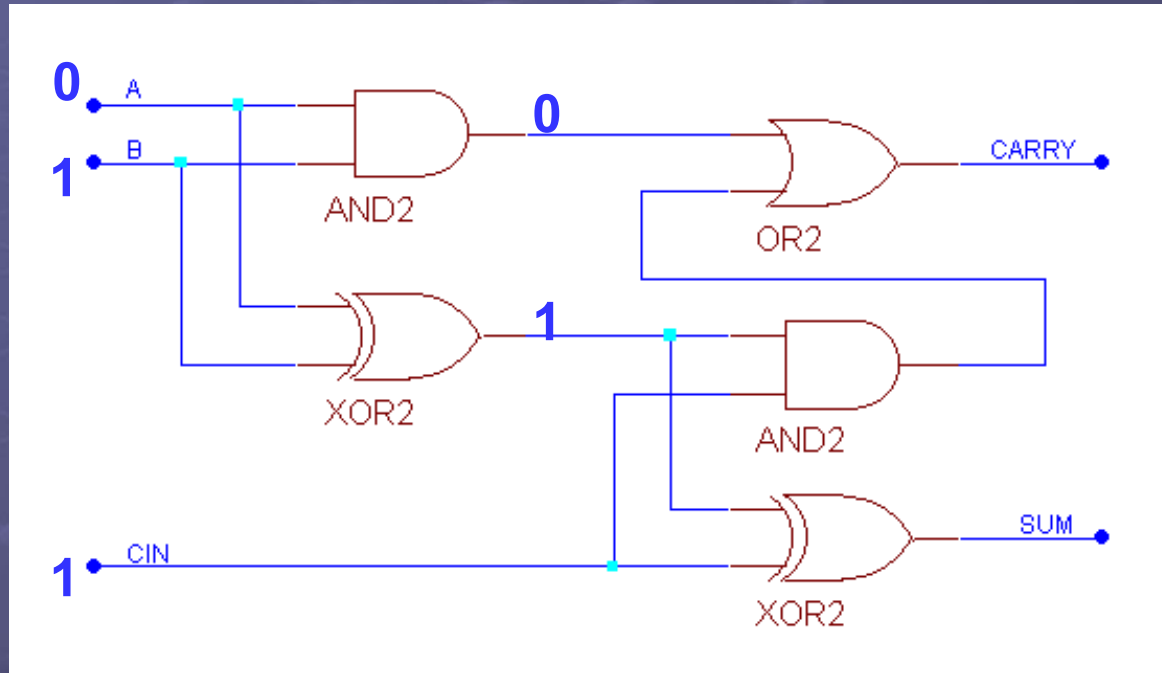

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

AND2

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1


OR2

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

XOR2

- Full Adder operation
 - ▶ Update outputs with stable values

Binary addition

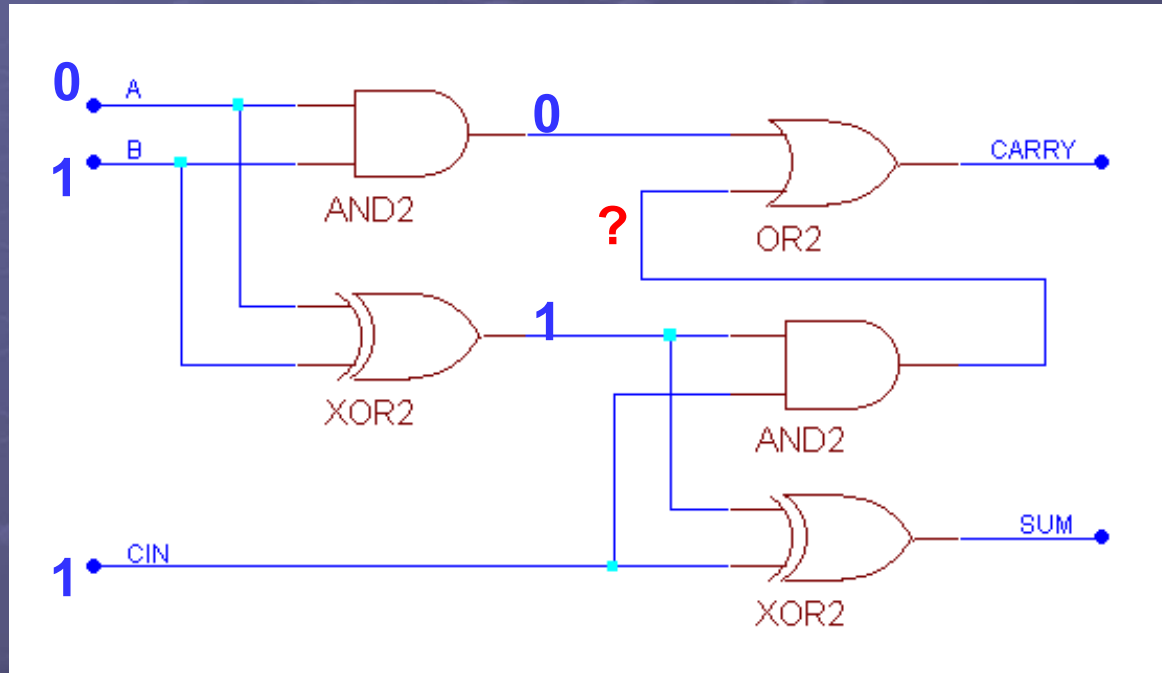

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

AND2

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1


OR2

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0


XOR2

- Full Adder operation
 - ▶ If input not known, trace signal back to source

Binary addition

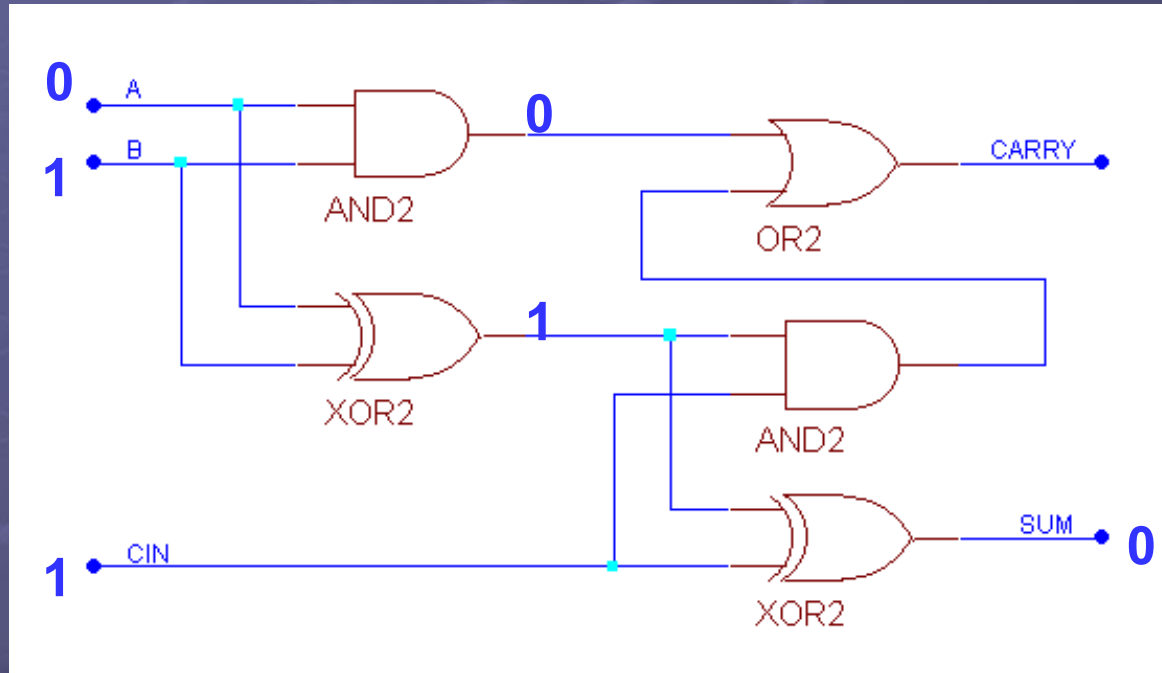

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

 

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1




A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0



- Full Adder operation
 - ▶ Update outputs with stable values

Binary addition

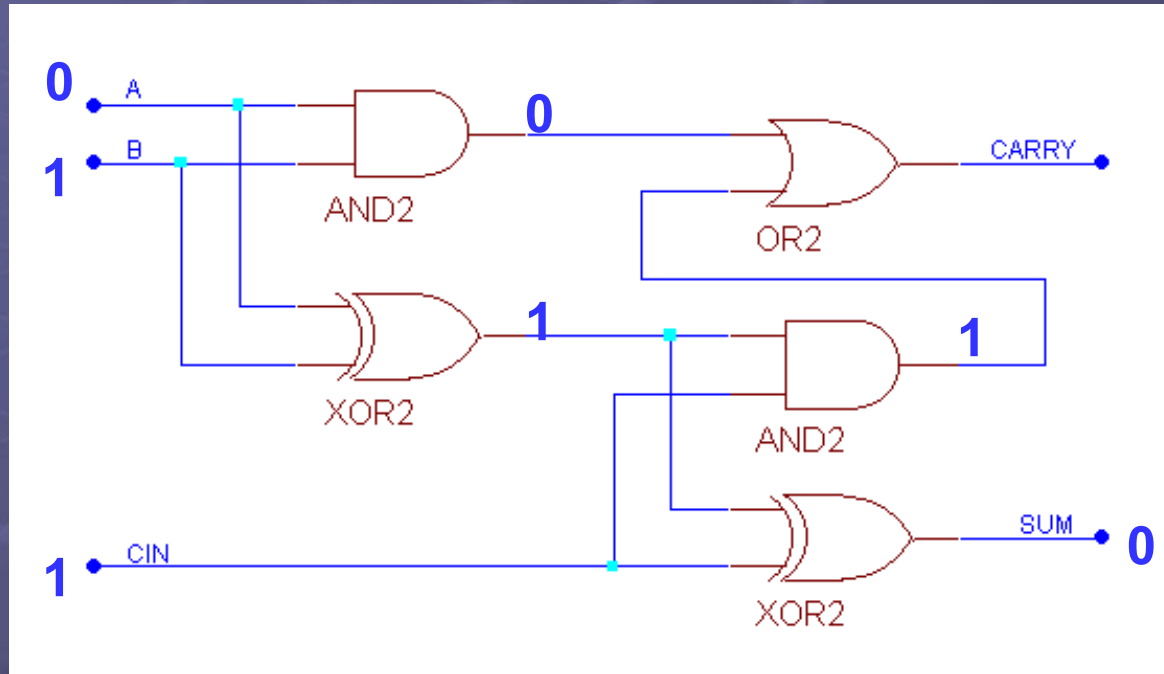

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

AND2

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1


OR2

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0


XOR2

- Full Adder operation
 - ▶ Update outputs with stable values

Binary addition

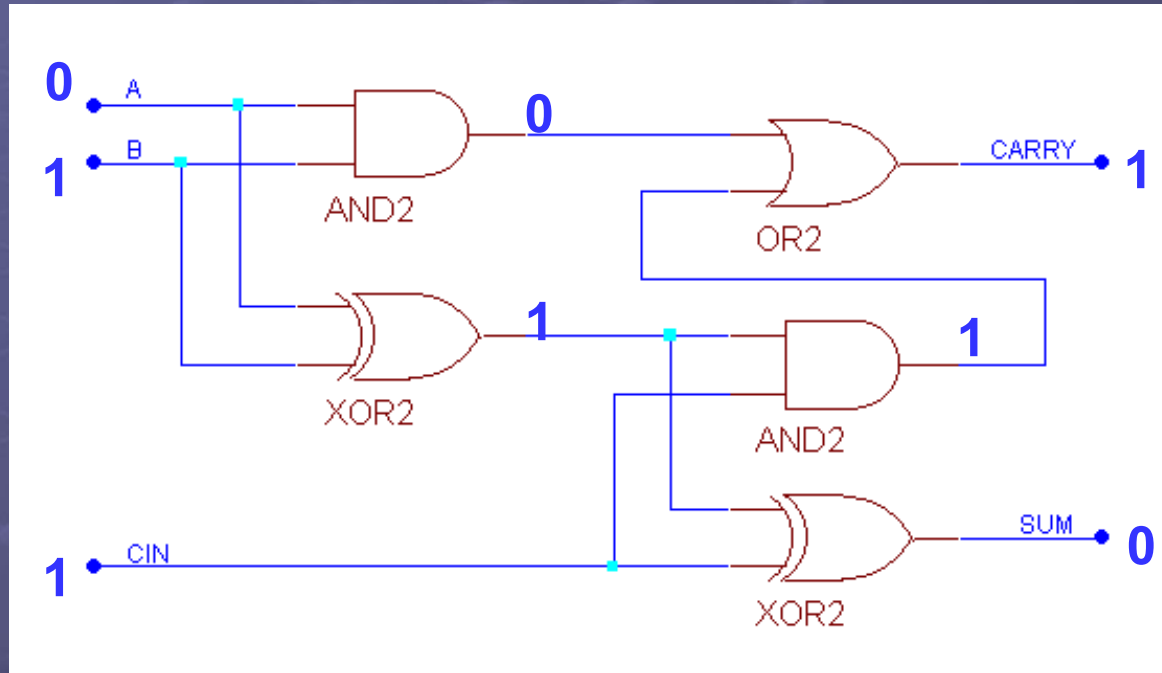

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

 

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1




A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0




- Full Adder operation
 - ▶ A=0, B=1, C=1
 - ▶ Sum=0, Carry=1

Binary addition

 

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

 

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1




A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0



- Important limitation : critical path
 - ▶ Worst case delay path, a signal needs to travel through three gate to produce a stable output.

Binary addition

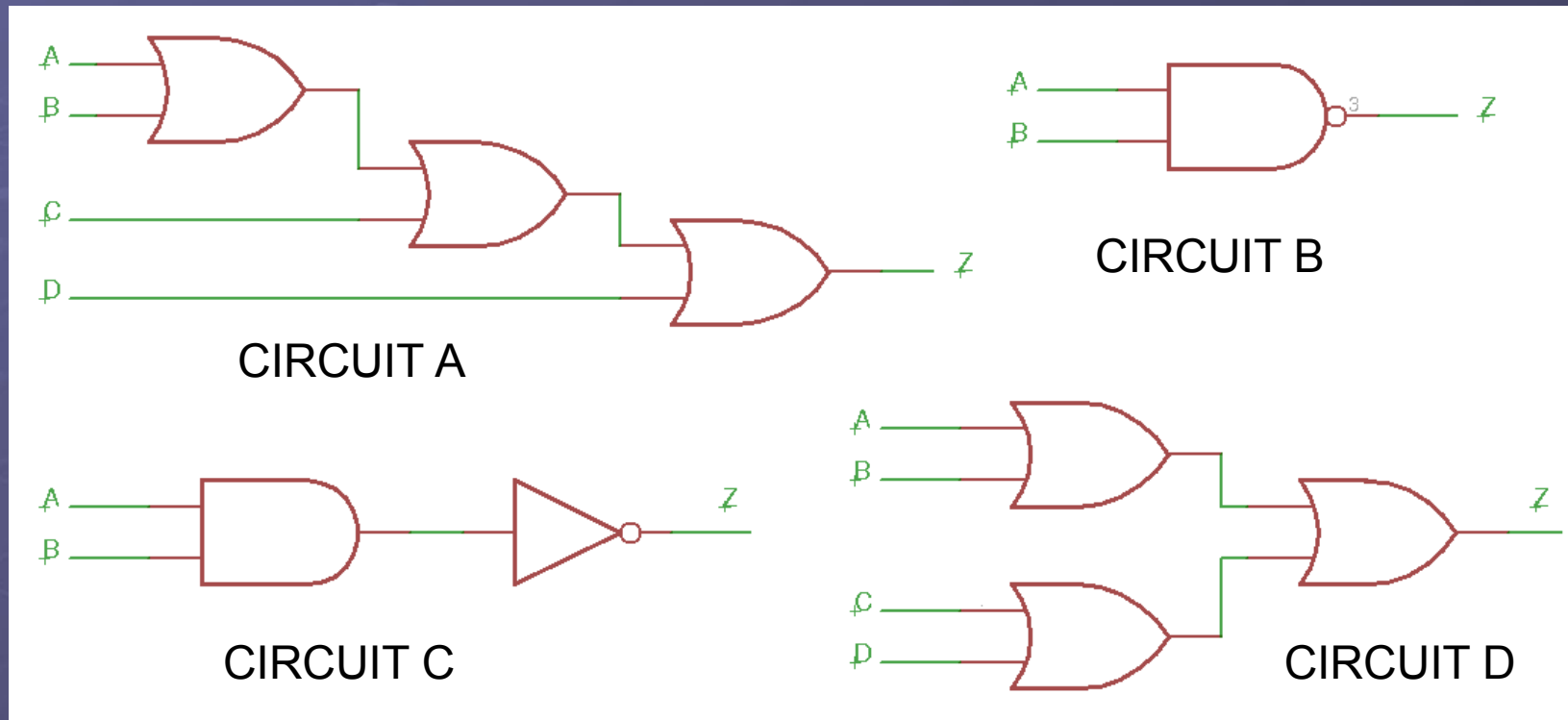

- Quick Quizzz

- ▶ Which rank these circuits in order of critical path delay, quickest to slowest.

Summary

- Key concepts :
 - ▶ Fundamental building blocks of a computer:
 - ◆ Multiplexer (bit and byte), Encoder, Decoder, Adder ...
 - ▶ Binary encodings
 - ◆ Binary, BCD, One-hot, Gray code ...
 - Link : https://en.wikipedia.org/wiki/Gray_code
 - ▶ Binary arithmetic
 - ◆ Half adder, Full adder, Ripple adder, Carry, Overflow.
 - ◆ Hardware limitations : Critical Path Delay (CPD)
 - Each logic gate will take some time to update its output for a change on its input i.e. propagation delay.
 - ▶ Operation of simple combinatorial logic circuits